




# (MAINLY) FOR FUN: HIGHER ORDER FILTERS



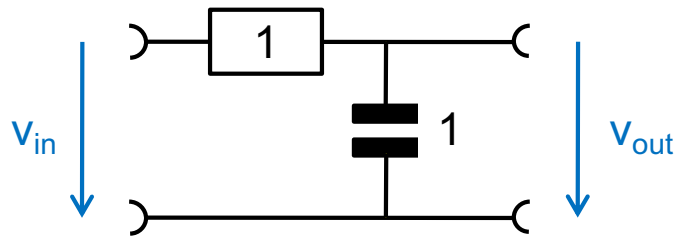
# Reminder: One Low Pass

- (For simplicity, we use fixed values for R and C, often 1  $\Omega$ /F)



$$H_{LP1}[s] = \frac{1}{1 + s}$$

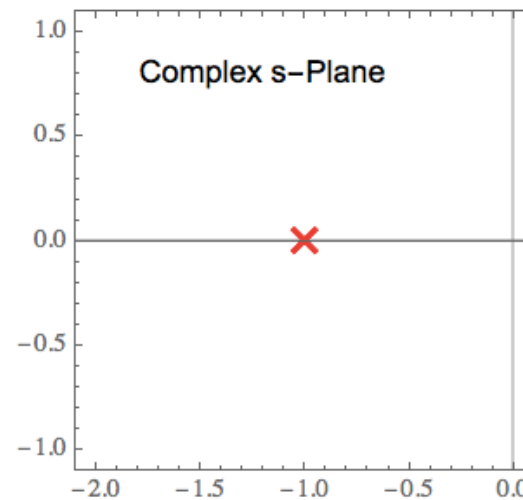- Mathematically, the function  $H_{LP1}[s]$  has a **POLE** at  $s = -1$ .
- This can be illustrated in the COMPLEX s-Plane:




- This particular pole is **real**, i.e. it lies on the real axis



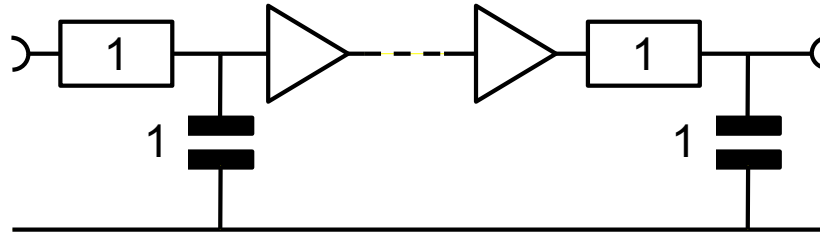
# Reminder: Cascaded Low Pass Stages

- If we cascade  $N$  stages *with buffers*, we get



$$H_{LPN}[s] = \frac{1}{(1 + s)^N}$$

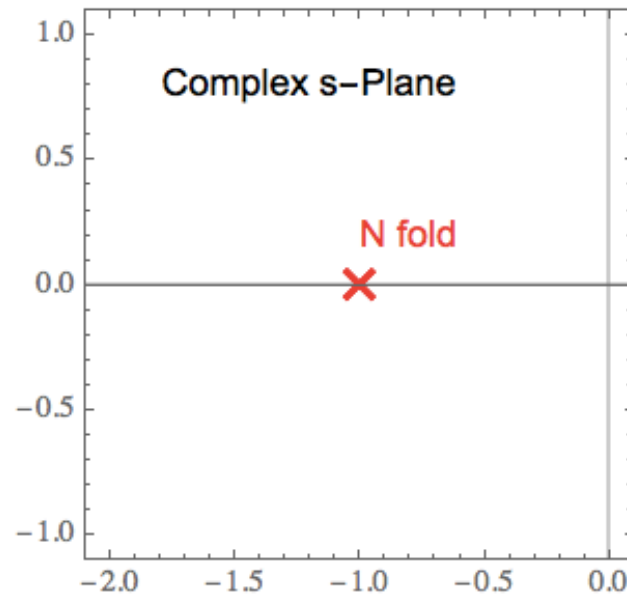
- $H_{LPN}[s]$  has a ***N-fold*** POLE at the same location  $s = -1$ .




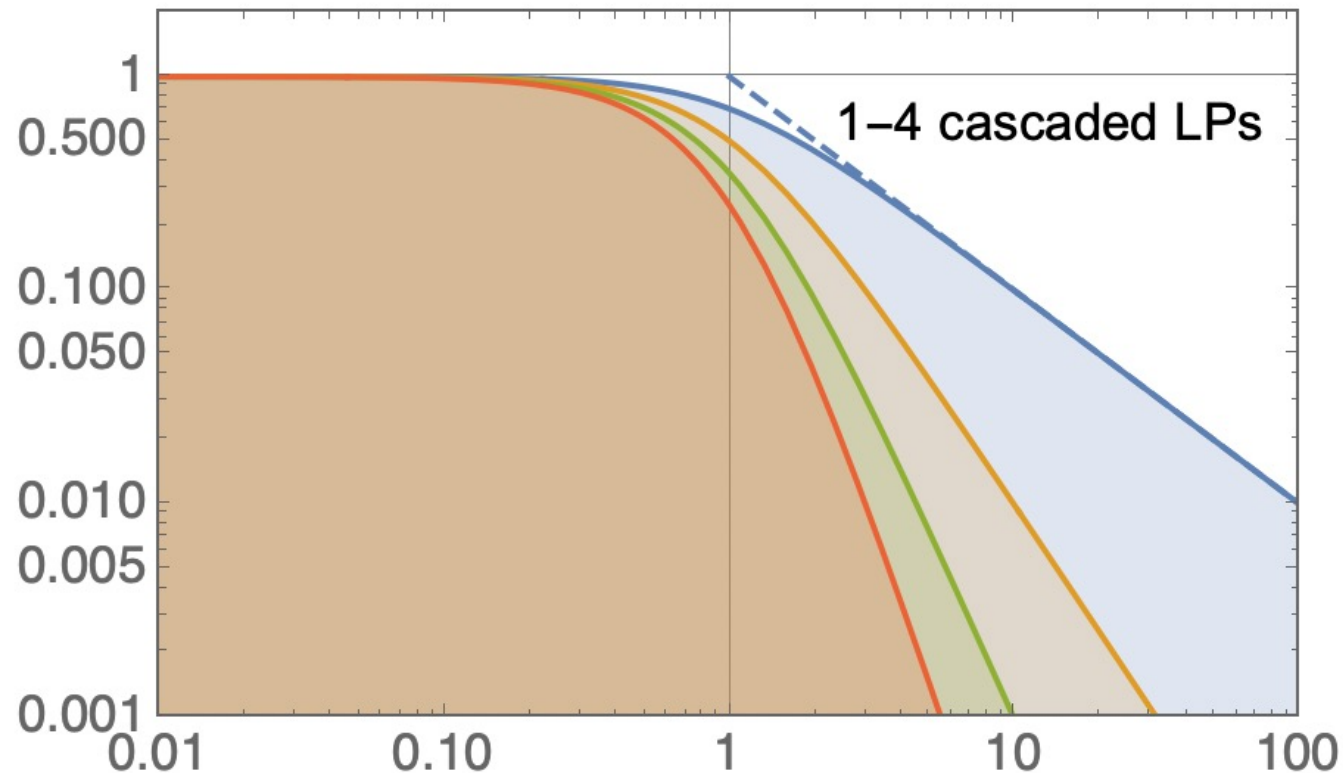
# Bode Plot of Cascaded Low Pass Stages


- The simple Low-Pass rolls off with 6dB/Octave (slope -1)
- Every further Low-Pass adds another 6dB/Octave




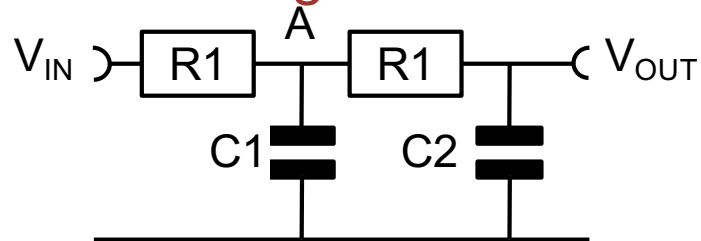
# Two Unbuffered Low Pass Stages

- If we cascade two stages *without a buffer*,



the transfer function gets more complicated.

$$EQ1 = \frac{v_{in} - v_A}{R1} = \frac{v_A - v_{out}}{R2} + v_A s C1; \quad (* \text{ node A } *) \quad EQ2 = \frac{v_A - v_{out}}{R2} = v_{out} s C2; \quad (* \text{ node Vout } *)$$

`Eliminate[{EQ1, EQ2}, vA] // Simplify`

$$v_{in} = (1 + C2 (R1 + R2) s + C1 R1 s (1 + C2 R2 s)) v_{out}$$

$$\frac{v_{out}}{v_{in}} /. \text{First@Solve}[\%, v_{out}]$$

$$\frac{1}{1 + C1 R1 s + C2 R1 s + C2 R2 s + C1 C2 R1 R2 s^2}$$


`% /. {R1 -> 1, R2 -> 1, C1 -> 1, C2 -> 1} // Highlighted`

$$\frac{1}{1 + 3s + s^2}$$



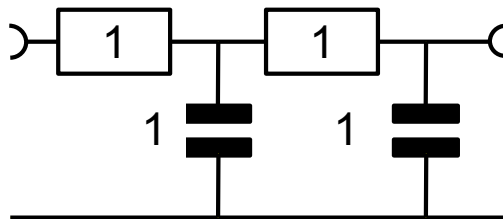
# Two Unbuffered Low Pass Stages

- For  $R_1=R_2=1$  and  $C_1=C_2=1$ , we get



$$H_{LPCasc}[s] = \frac{1}{1 + 3s + s^2}$$

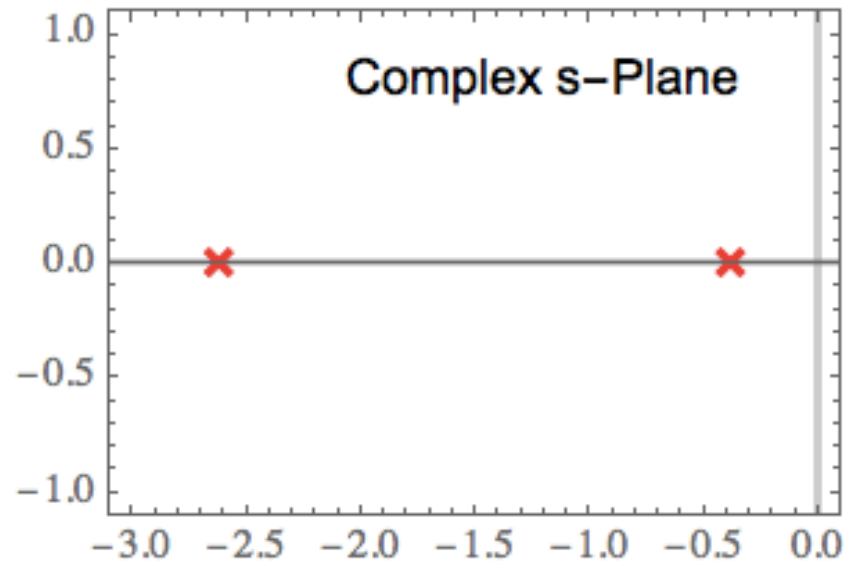- We now have *two different* (still real) poles:




(Their exact locations depend on R/C ratios..)



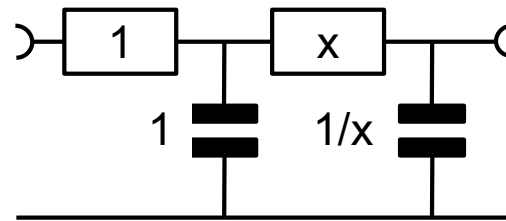
## (Pole Location for Previous Case)

- If we modify R,C of the second stage, keeping  $RC = 1$ , we get



$$H[s_] = \frac{x}{s + x + 2sx + s^2x}$$

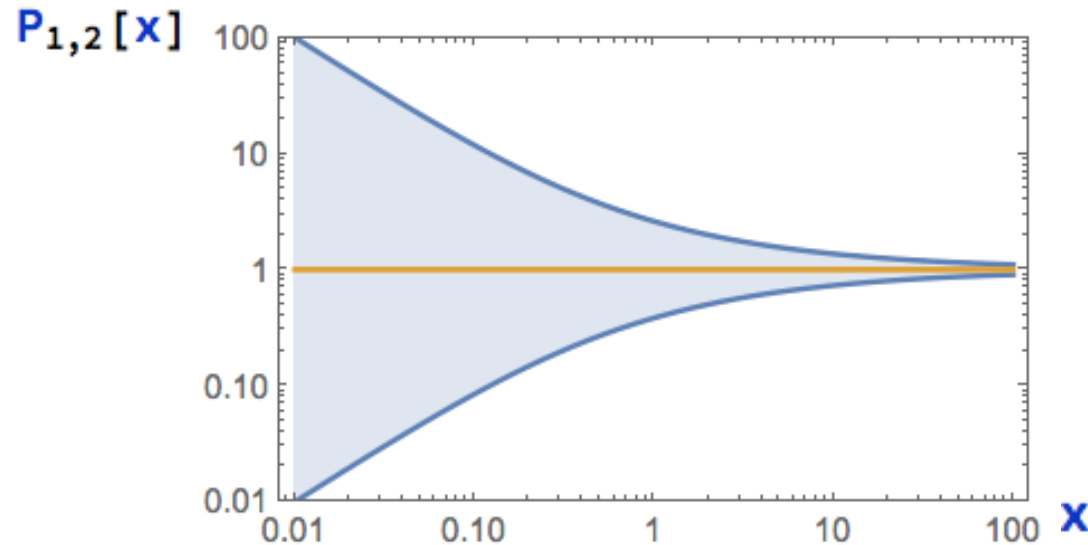- The poles are at  $P_{1,2}[x] = \frac{-1 - 2x \pm \sqrt{1 + 4x}}{2x}$




(when  $x$  is large, the 2<sup>nd</sup> LP does not load the 1<sup>st</sup>)


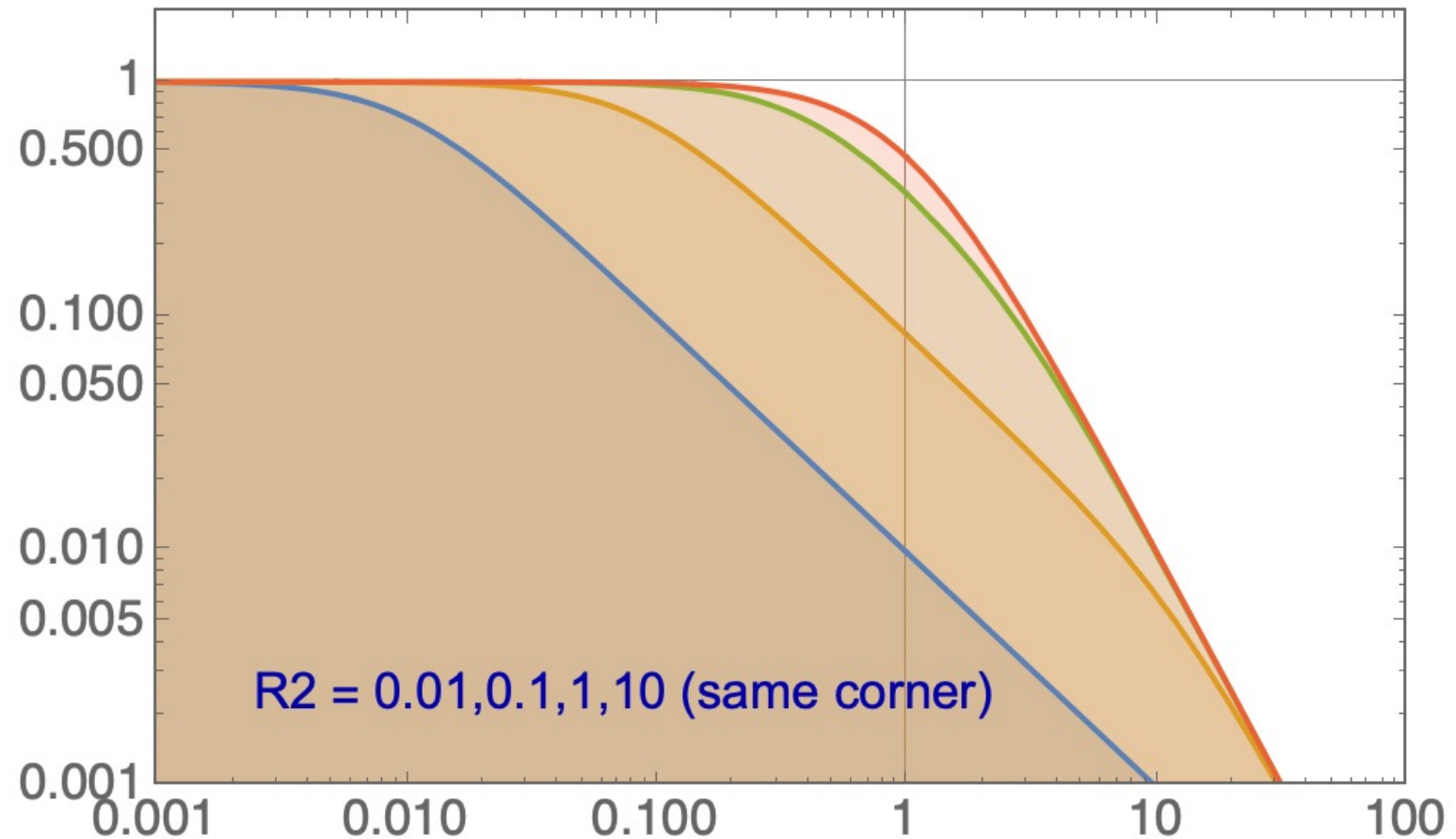
# Bode Plot of 2 Unbuffered Low Pass Stages

- The 2 different real poles lead to kinks at two frequencies







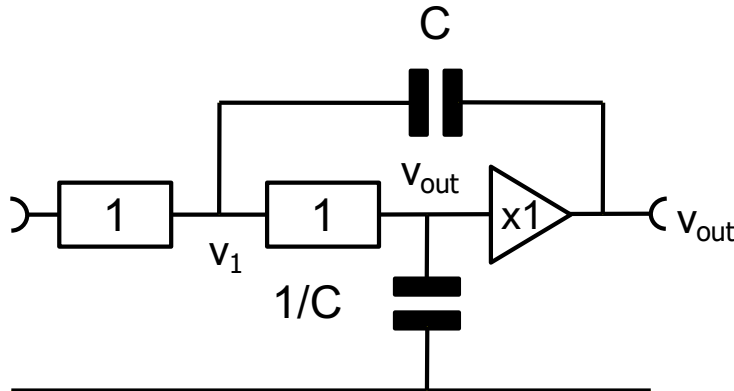
# An Active Filter

- Now consider the following filter ('Sallen and Key')





$$EQ1 = \frac{v_{in} - v_1}{1} == \frac{v_1 - v_{out}}{1} + (v_1 - v_{out}) s 10;$$

$$EQ2 = \frac{v_1 - v_{out}}{1} == v_{out} s \frac{1}{10};$$

for C=10

$$H[s] = \frac{5}{5 + s + 5 s^2}$$

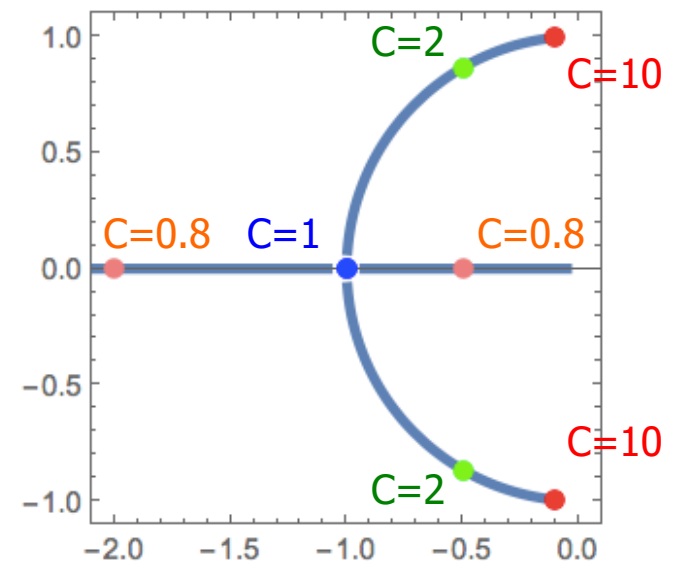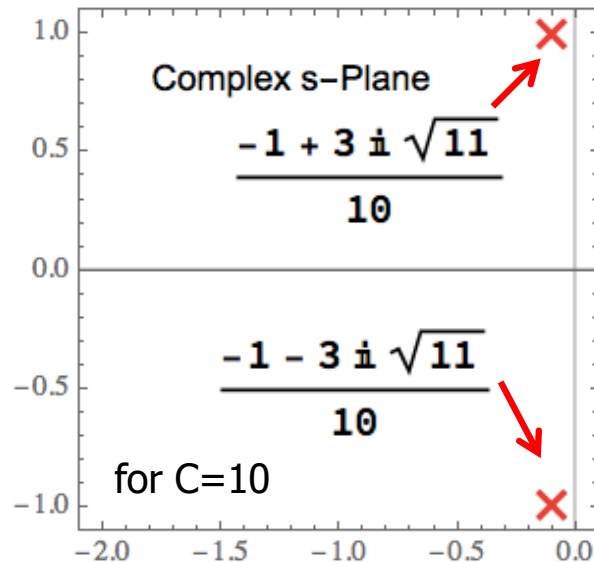
- This transfer function has two **COMPLEX** (conjugate) poles:




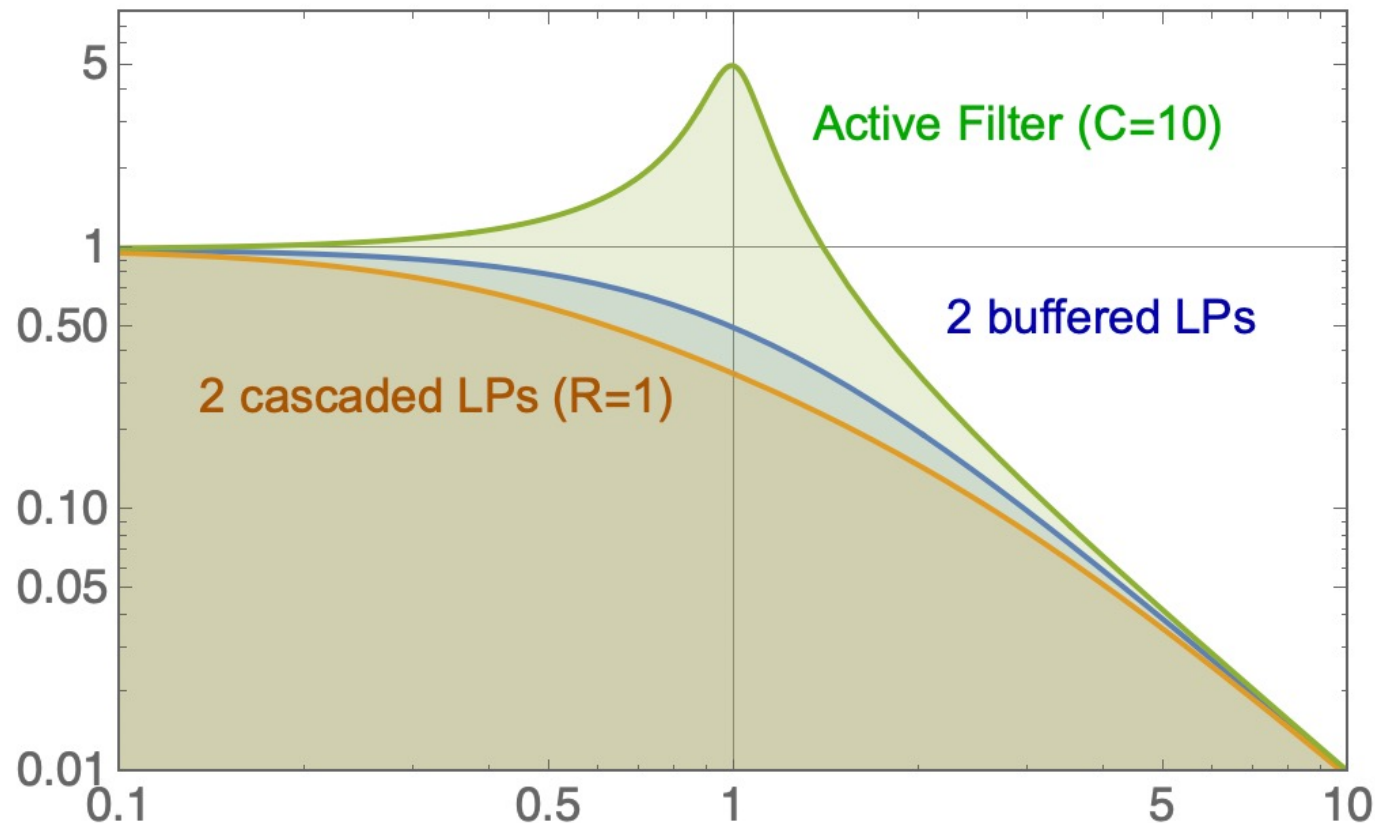
# Bode Plots of 2nd Order Filters

- The active filter has an overshoot (for the values chosen)
- This is typical for complex conjugate poles






# MAKING STEEP FILTERS


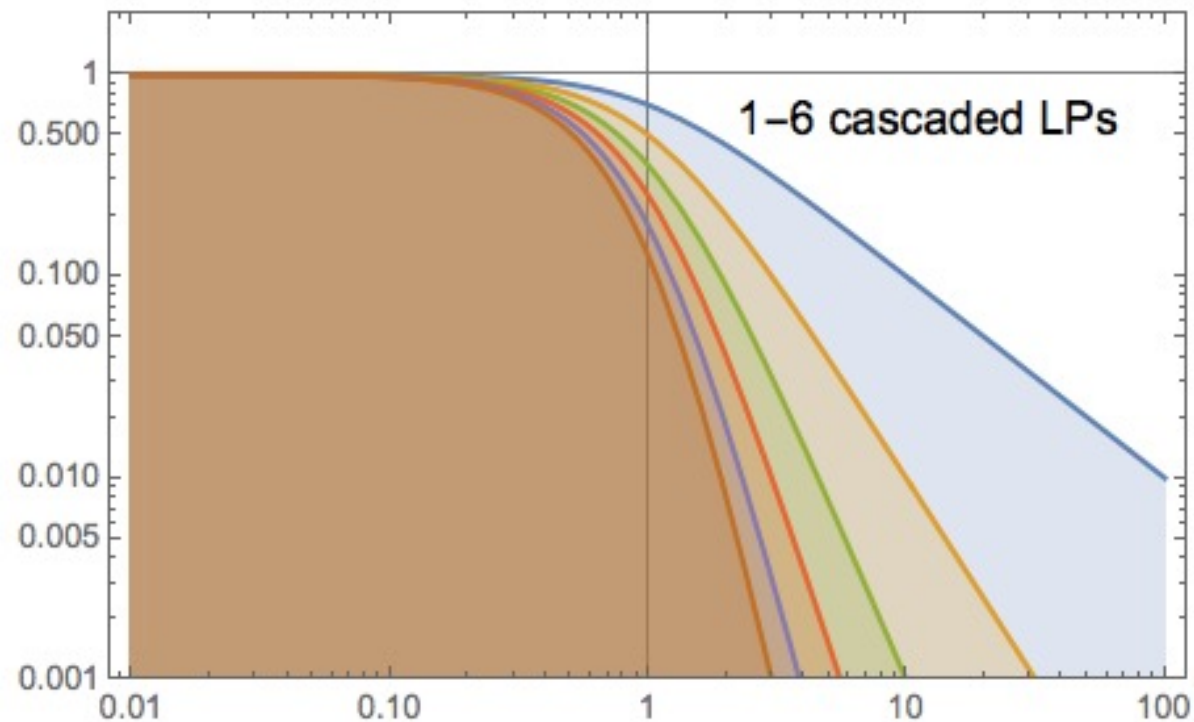
# A Steep Low Pass Filter

- We want to design a higher ( $N^{\text{th}}$ ) order low-pass filter which drops suddenly from **pass band** to **stop band**.
- We know that we roll off with slope  $-N$  at the end (for  $s \rightarrow \infty$ ).




- Simple cascaded LPs attenuate by  $2^{-N/2}$  at the corner
- Can this be improved ?



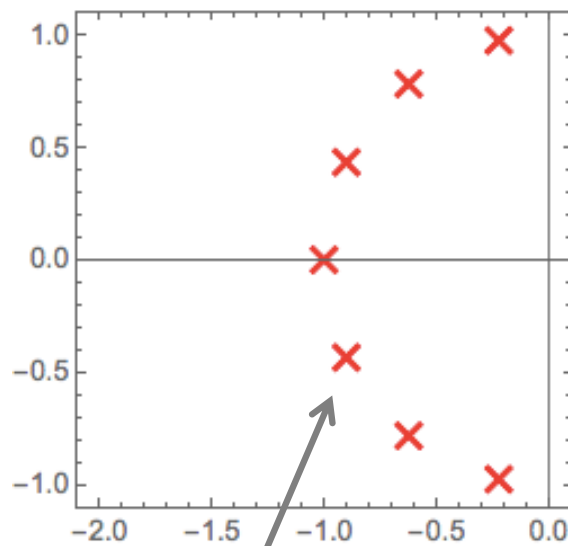
# Choosing the Poles

- The Idea: Use complex poles and adjust them 'somehow'
- 'Butterworth' arranges poles on circle. Here: 7<sup>th</sup> order.



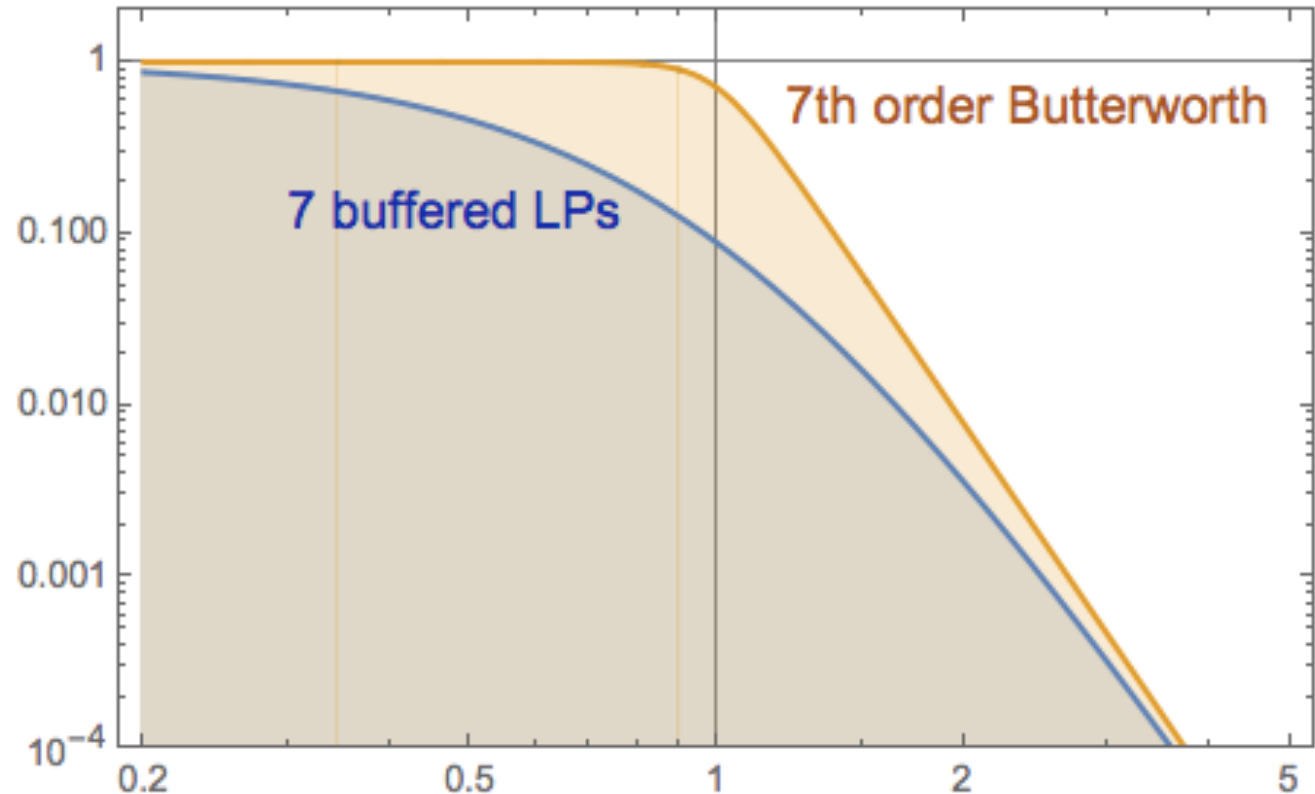It can be shown (easily) that poles on a circle have same corner frequencies.





- Wow! Butterworth attenuation at the corner is only -3dB !


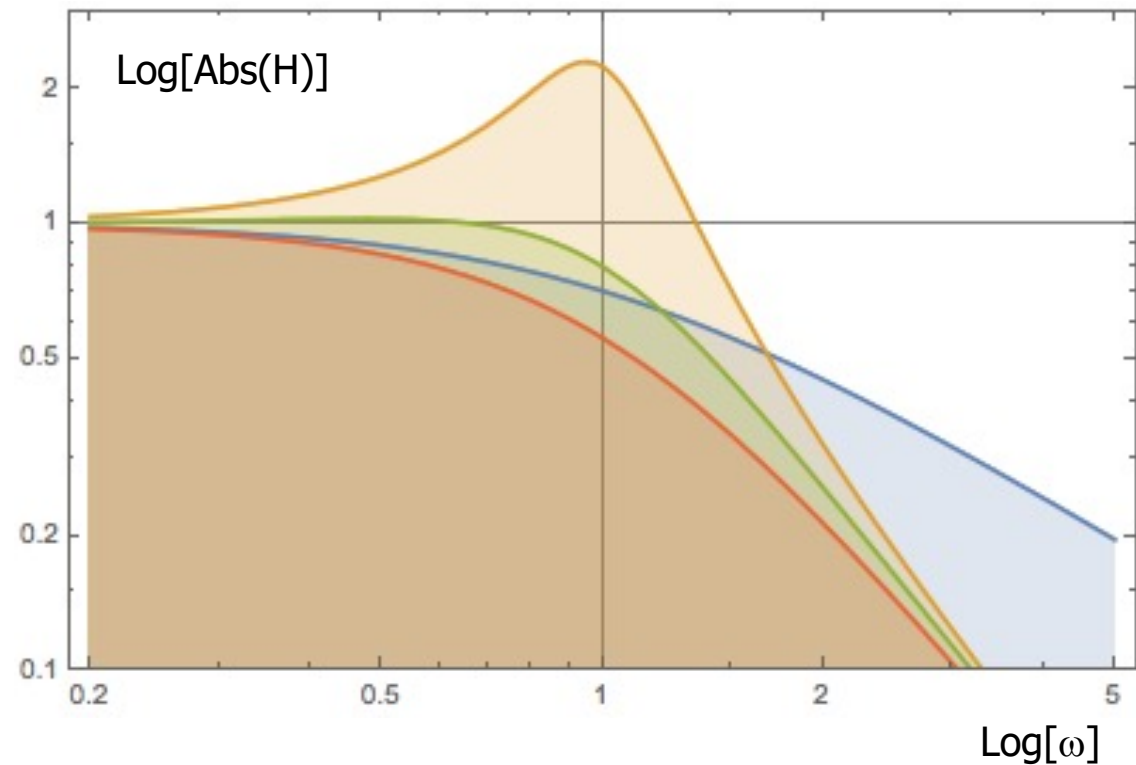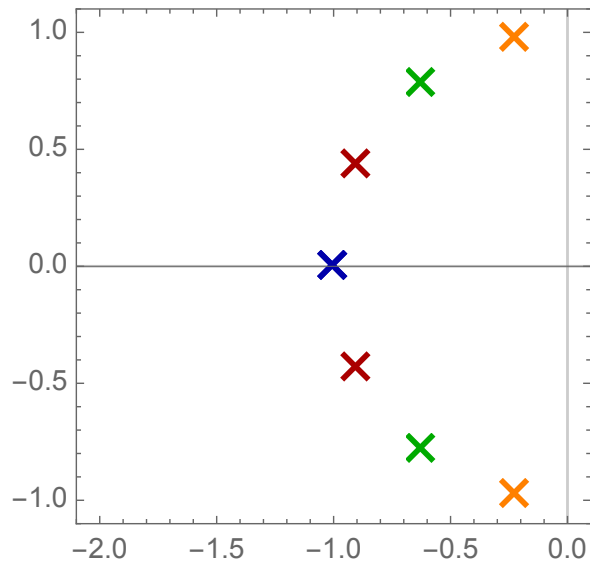
# (Decomposing the Butterworth Filter)


- For  $N=7$ :
  - One real pole (1<sup>st</sup> order, blue)
  - 3 conjugate poles (2<sup>nd</sup> order)




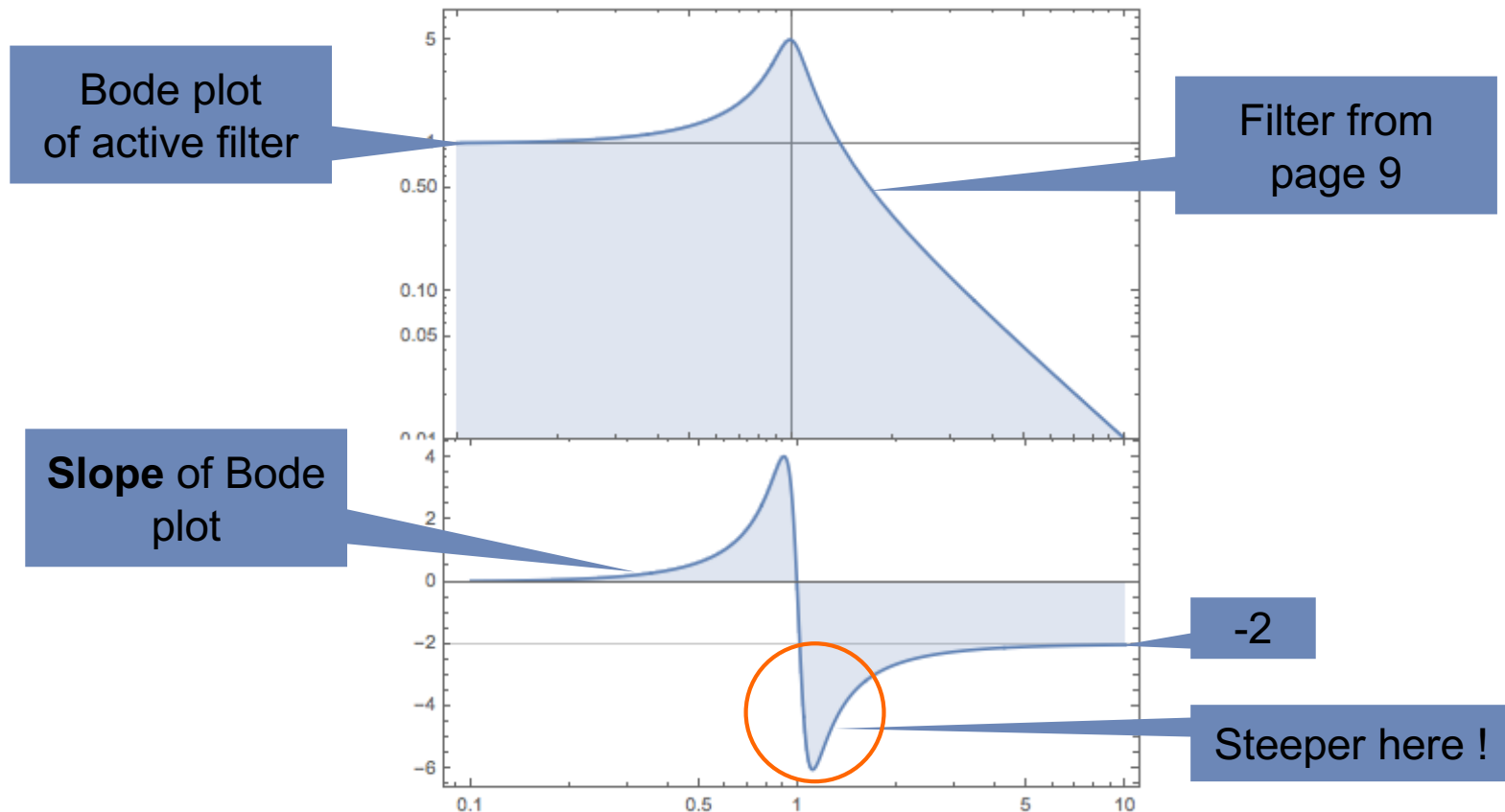
# Even Steeper?

- Remember: For *large* frequencies, we will *always* roll off with  $s^{-N}$  (the order of the filter, i.e. the number of caps)
- But: The 'peaking' for complex poles provides steeper response *close to the bandwidth*:






## Placing the Poles...

- There are obviously MANY possibilities to place the poles...
  
- Desired filter properties are for instance
  - Flatness/ripple of the response in the pass band
  - Steepness of the drop
  - Ripple in the stop band
  - Response to step signals (overshoots)
  - Phase behavior
  
- Four main types have evolved:
  - Butterworth: Flat pass band
  - Bessel: No phase shift, no overshoot
  - Chebyshev: Steeper roll off, but ripple in pass band
  - Elliptic: Even steeper roll off, but ripple in pass and stop band






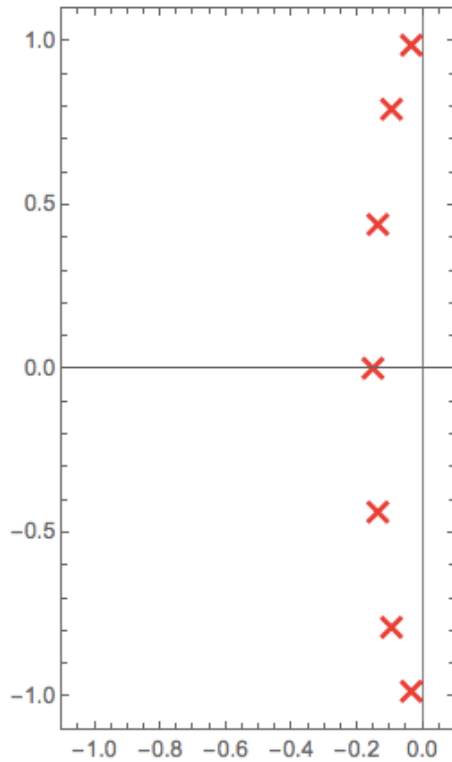
# Example: A Chebyshev Filter (7<sup>th</sup> order)



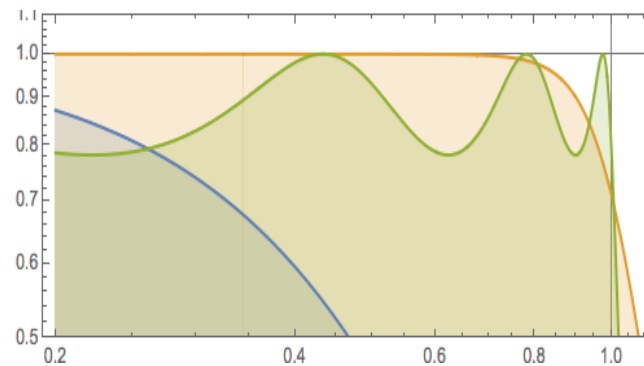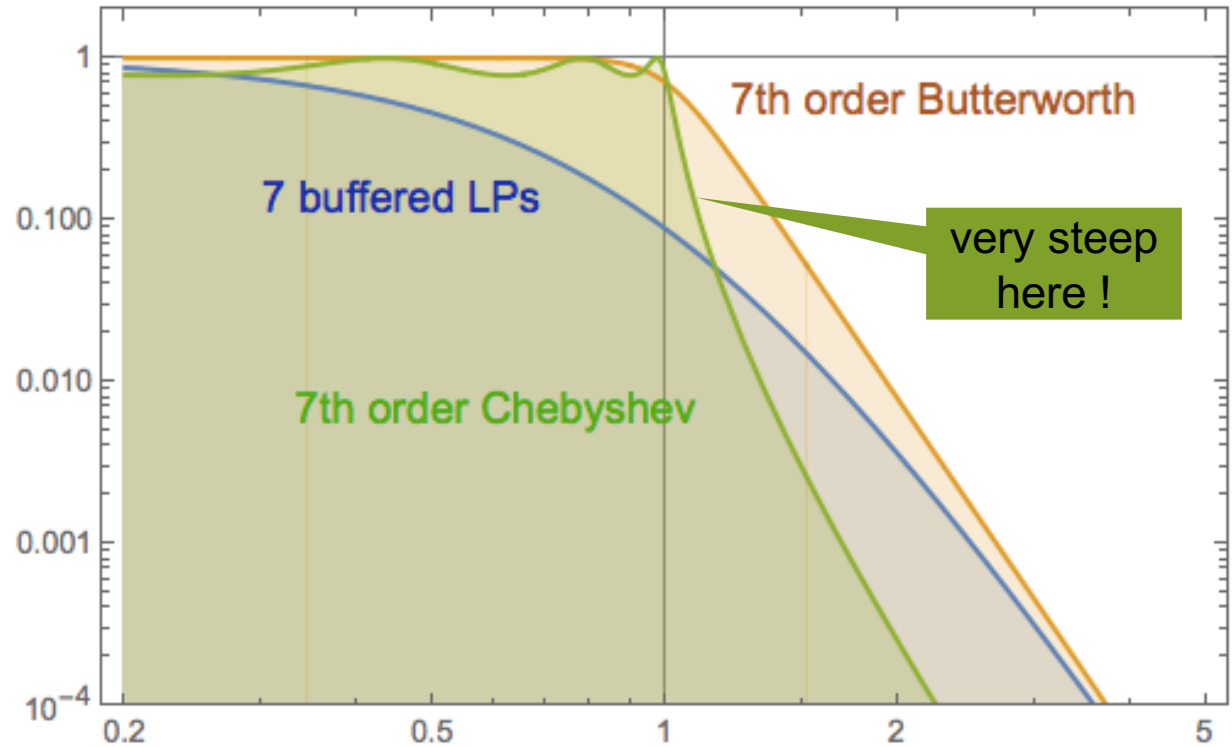Pole location for a 7<sup>th</sup> order Chebyshev filter (there are others, depending on the desired pass band ripple)



Zoom of pass band showing ripple of Chebyshev and flat response of Butterworth