




# The Gain Stage (Common Source Amplifier)

Finally: a voltage amplifier



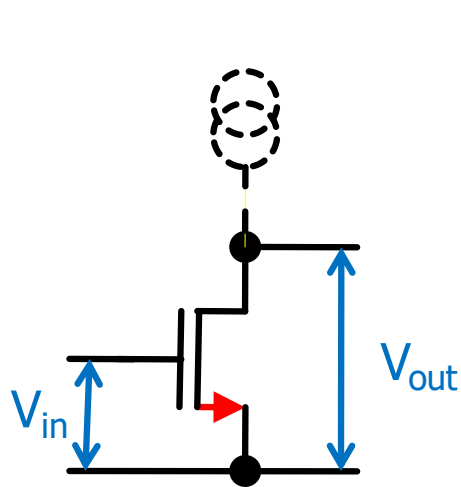
# The Three Basic Configurations:


- ‘Common **xxx** configuration’ means:  
Terminal **xxx** of the MOS is common to input and output



 - common **source** config.
- ‘gain stage’
- inverting **voltage gain**
- *high* input impedance
- *high* output impedance



 - common **drain** config.
- ‘source follower’
- voltage gain  $\leq 1$
- *high* input impedance
- **low** output impedance



- common **gate** config.
- ‘cascode’
- current gain = 1
- **low** input impedance
- *high* output impedance



# DC BEHAVIOR OF THE GAIN STAGE



# The Principle


- The current in the MOS is set mainly by the (large signal)  $V_{GS} = V_{in}$ , but also by  $V_D = V_{OUT}$
- We sent a constant current  $I_0$  to the drain from a (for now) *ideal* current source
- In the operation point,  $V_{GS}$  and  $I_0$  must ‘correspond’!

- When  $V_{in}$  **raises** (above the op. point)

- $I_D$  increases. It becomes  $> I_0$
- Current is pulled out of the load
- $V_{out}$  **drops**

- When  $V_{in}$  **drops**

 - $I_D$  decreases. It becomes  $< I_0$
- Current is pushed into the load
- $V_{out}$  **increases**



Inverting amplifier



# Large Signal Behavior

- Use real current source now (PMOS mirror)
- Observe the 4 main operation regimes:

$V_{in}$  is below NMOS threshold. No current in NMOS. PMOS can pull the output all the way to the positive supply 'VDD'


The NMOS starts to draw current. The PMOS is in the linear region, its output resistance is low, gain is low.

Both MOS are in saturation.

Gain is high.

We want to operate somewhere on this steep slope!

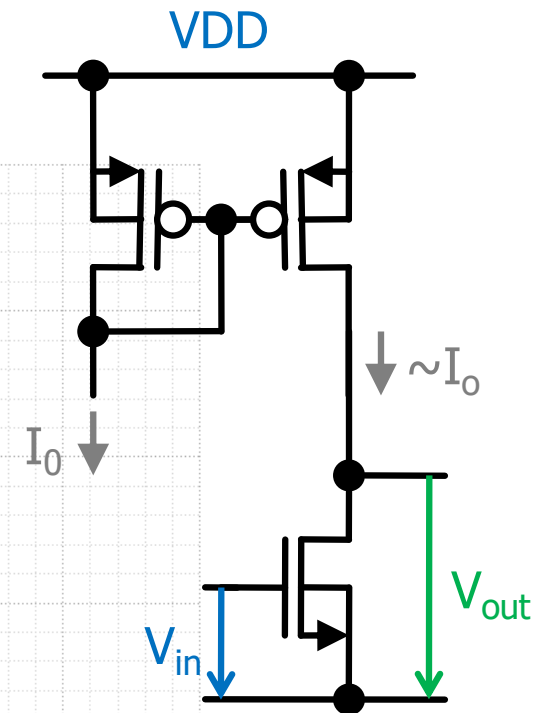
The drain voltage of the NMOS becomes too small. It goes into the linear region. Gain drops. Note that  $V_{out} = 0$  is *never* reached




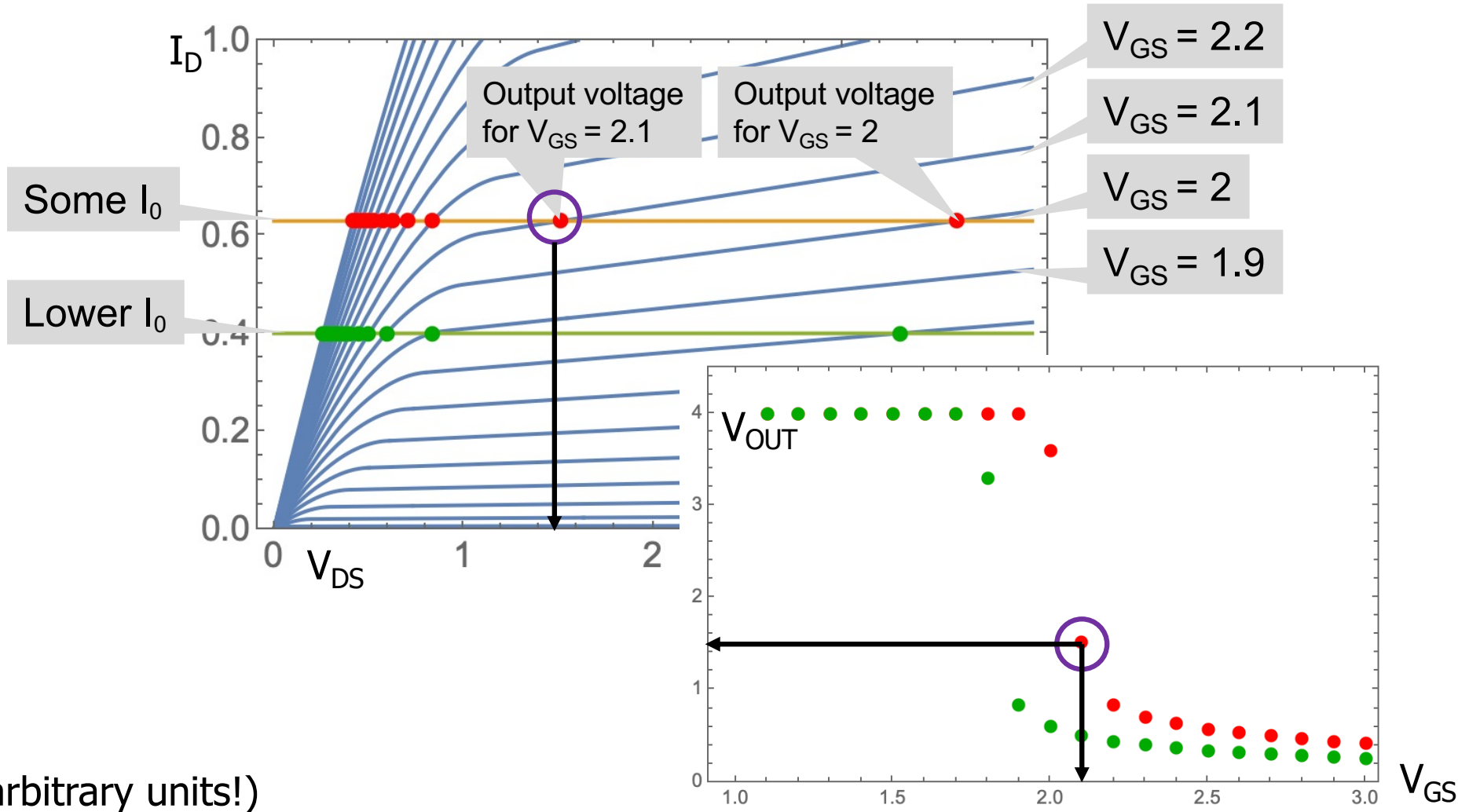
# Understanding the Curve

- The (blue) output characteristic ‘increases’ with  $V_{GS}$
- The output voltage settles where  $I_D = I_0$




(arbitrary units!)


 
# Changing the Bias Current

- For **more** bias current ('stronger current source'):




- 'Threshold' is 'later'
  - $V_{IN}$  must be higher until  $I_D$  reaches  $100 \mu A$
- 'Round region' is wider
  - The PMOS is longer in linear region because its  $V_{GS}$  is higher
- Output does not go so low (towards GND)
  - NMOS cannot deliver enough (relative to  $100 \mu A$ ) current, it comes into the linear region

Therefore, the DC operation point of  $V_{in}$  must be adjusted!


 
# The gain

- A small change in  $V_{in}$  leads to a large change in  $V_{out}$  if the transfer curve is steep.
- The gain is the derivative of  $V_{out}(V_{in})$
- NOTE that the gain is different along the curve, i.e. for different  $V_{in}$ !!  
It depends on the operation point!







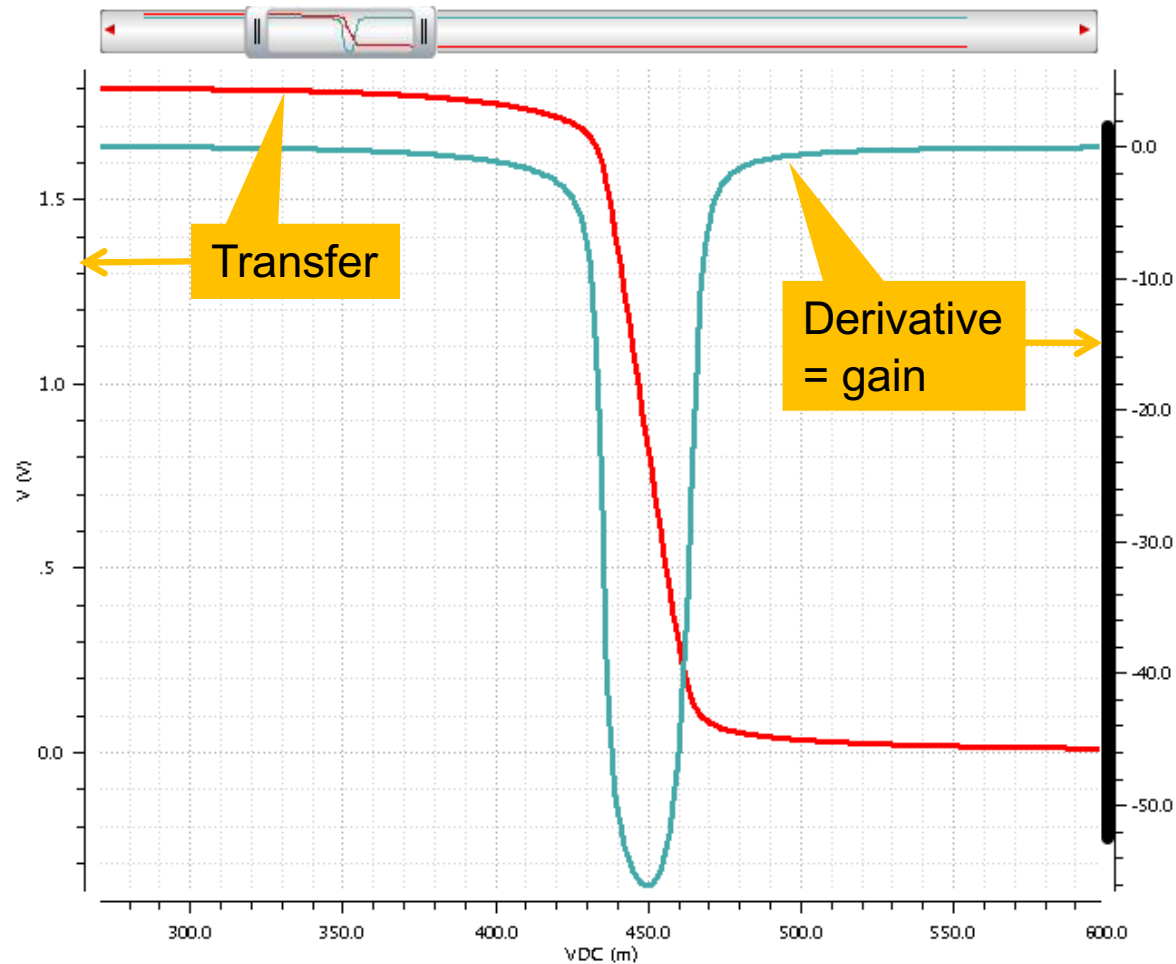
# Gain vs. $V_{IN}$


- Can be obtained by taking derivative of transfer curve




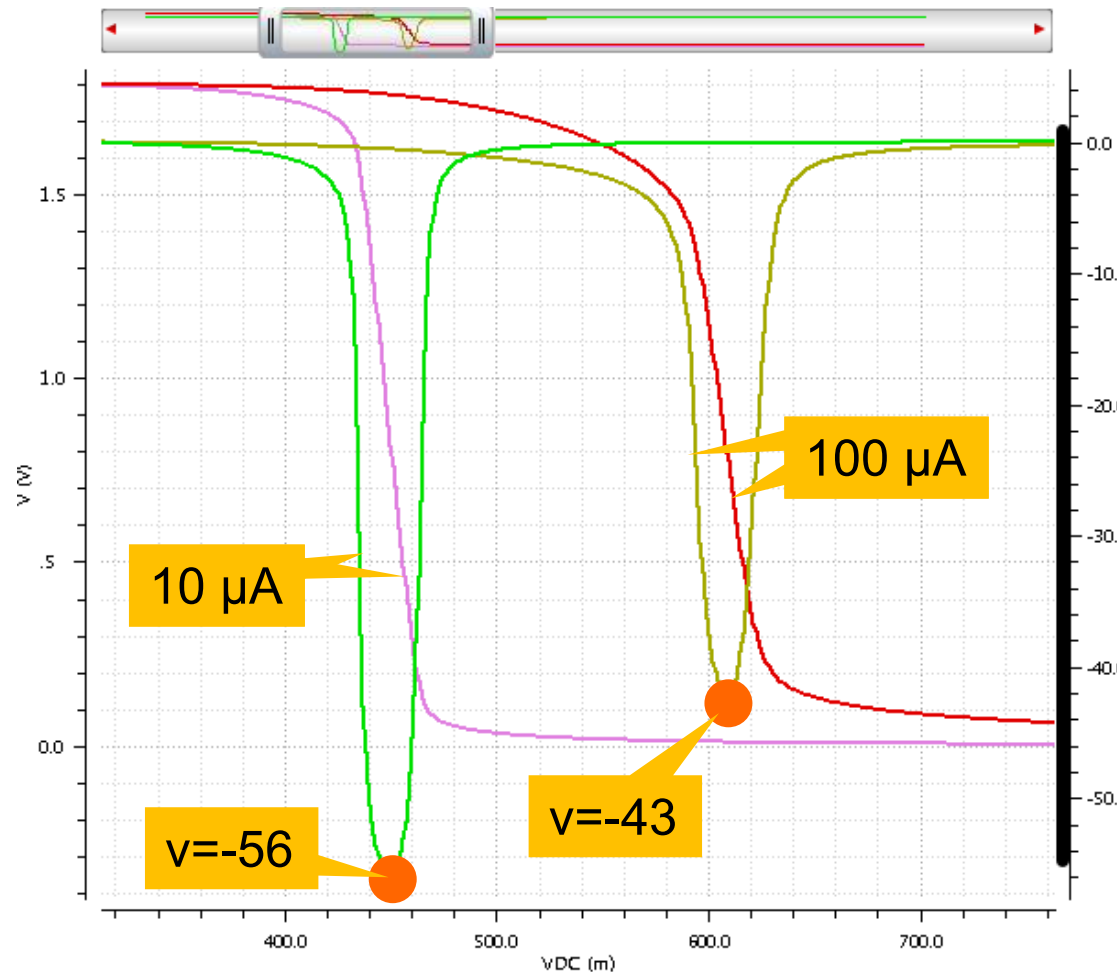
# Gain at Different bias Currents


- Position of 'maximal gain' *depends on bias current*
- Max. gain is lower for high current (we will understand why!)




 
# Gain of the Gain Stage: Intuitive Way

- When  $V_{in}$  changes by a small amount  $\Delta V_{in} = v_{in}$ , how much does  $V_{out}$  change, i.e. what is  $v_{out}$ ?
  - Note difference in Capital and Small letters:  $V_{in} \neq v_{in}$
  - Capitals: Large signal, small: small signal



- What happens?
  - $v_{in}$  leads to a change  $i_D$  of  $I_D$  of  $i_D = g_m v_{in}$  (Definition of  $g_m$ !)
  - With a resistive load  $R$ , this gives a voltage change  $v_{out} = R \times i_D$
  - This change is opposite in direction to  $v_{in}$
  - Therefore:  $v_{out} = - R \times g_m \times v_{in}$


$$\text{gain } v = v_{out}/v_{in} = - R \times g_m$$


 
# Gain of the Gain Stage: Small Signal Calculation

- Consider only the MOS (i.e. use ideal current source for bias)
- Replace MOS by its small signal equivalent:

We assume that **no** current flows to output!



## ▪ Calculation

- current at output node = 0 (Kirchhoff)
- therefore:  $0 = g_m \times v_{in} + v_{out} / r_{ds}$

- so that  $v = v_{out}/v_{in} = -g_m \times r_{ds}$  as before!



# Numbers

- Typical gains are 10 ... 40
  - they depend on technology, current, transistor size,...

- Therefore:  $|v| = g_m r_{ds} = g_m / g_{ds} > 10 \gg 1$

or  $g_m > 10 / r_{ds} = 10 g_{ds}$

The transconductance  $g_m$  of a MOS is usually much larger than the output conductance  $g_{ds}$ .

- This can often be used to simplify small signal expressions!



## Comparing to 'abstracted circuits'

- The difference to the 'abstract circuits' exercise is that the 'current source' in the NMOS
  1. does not provide 'negative' current when  $V_{IN}$  is negative  
-> output cannot rise above VDD
  2. does not provide current any more when  $V_{OUT}$  is small (MOS gets out of saturation)  
-> output cannot fall below GND
  
- The analogy is in the steep, central part
  
- There is an offset created by the threshold voltage




# AC BEHAVIOR OF THE GAIN STAGE


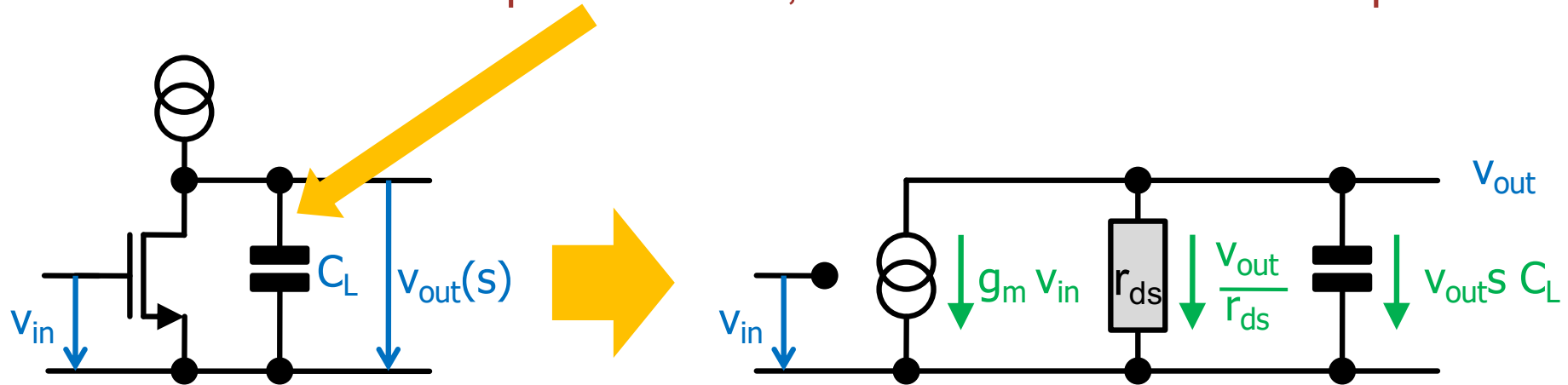
# Adding a Capacitive Load – ‘The Speed’

- With a capacitive load, we have another current path:



- Current sum at output node = 0:  

$$0 = g_m v_{in} + v_{out} / r_{ds} + s C_L v_{out}$$

$$v(s) = - \frac{g_m r_{ds}}{1 + s r_{ds} C_L}$$


DC gain (as before)

Low pass behavior  
 Corner at  $1/(r_{ds} C_L)$





# Bode Plot of the Gain Stage

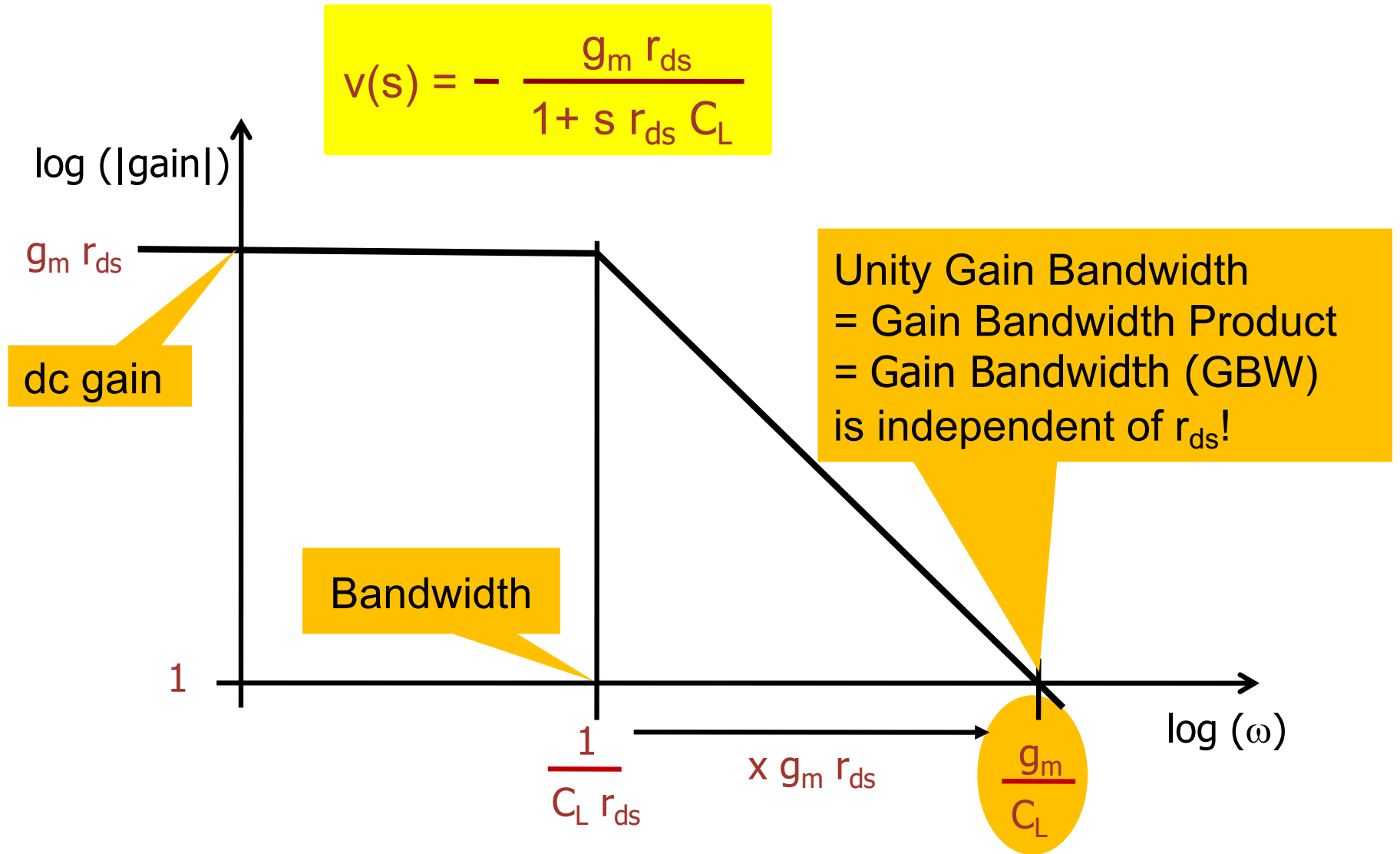



# Remember: Gain-Bandwidth-Product


$$\text{GBW} = \frac{g_m}{C_L}$$

$$v = - \frac{g_m r_{ds}}{1 + s r_{ds} C_L}$$


 
# Bode Plot for two current

- Increasing  $I_D$ 
  - increases  $g_m$  and thus GBW
  - decreases  $r_{ds}$  and thus dc gain





# Increasing the gain

- The gain of a single MOS is  $v = g_m r_{ds}$ .
- $g_m \sim \text{sqrt}[2 K I_D W/L]$  (strong inversion)
- $r_{ds} \sim L / I_D$



	$I_D \rightarrow 2 I_D$ (strong inv.)	$I_D \rightarrow 2 I_D$ (weak inv.)	$I_D \rightarrow 2 I_D$ (vel. sat.)	$W \rightarrow 2 W$ (s.i.)	$L \rightarrow 2 L$ (s.i.)
$g_m$	$\rightarrow \sqrt{2} g_m$	$\rightarrow 2 g_m$	$\rightarrow g_m$	$\rightarrow \sqrt{2} g_m$	$\rightarrow g_m / \sqrt{2}$
$r_{ds}$	$\rightarrow r_{ds} / 2$	$\rightarrow r_{ds} / 2$	$\rightarrow r_{ds} / 2$	$\rightarrow r_{ds}$	$\rightarrow 2 r_{ds}$
$v$	$\rightarrow v / \sqrt{2}$	$\rightarrow v$	$\rightarrow v / 2$	$\rightarrow \sqrt{2} v$	$\rightarrow \sqrt{2} v$

- We see:
  - gain is *increased* by *larger*  $W$  or  $L$  and by *smaller*  $I_D$
  - *gain-bandwidth* only depends on  $g_m$ , i.e. mainly on  $I_D$


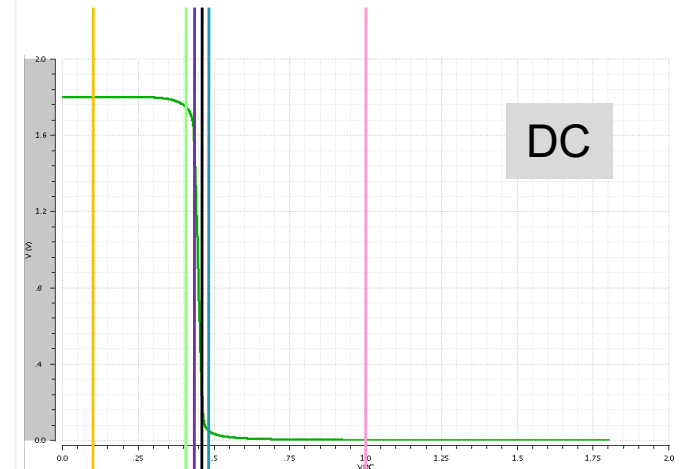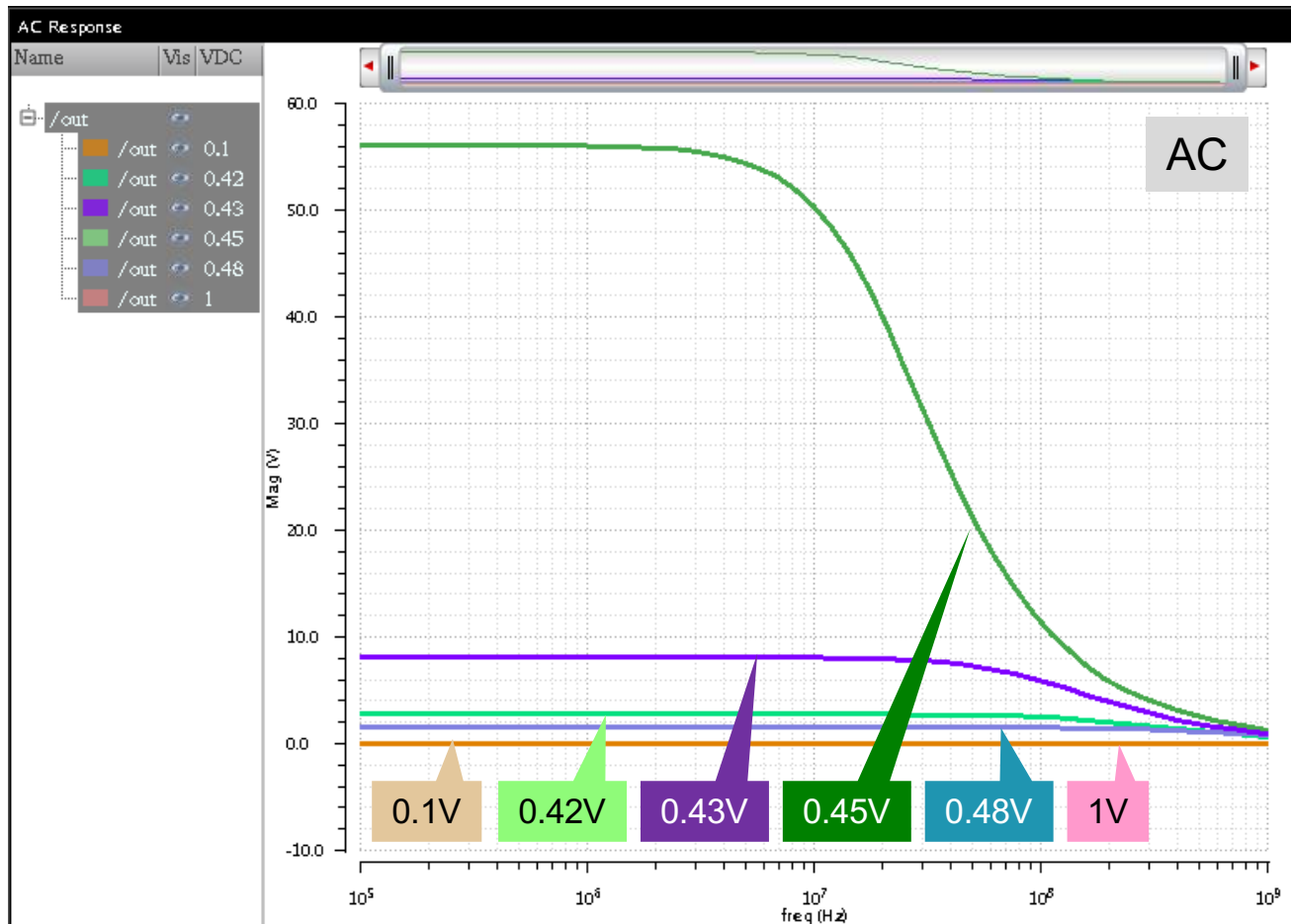
# AC sweeps at different Operation Point

- It the DC potential of  $V_{IN}$  is changed, we move to different points of the transfer curve:




Transfer Curve with the chosen Operation points


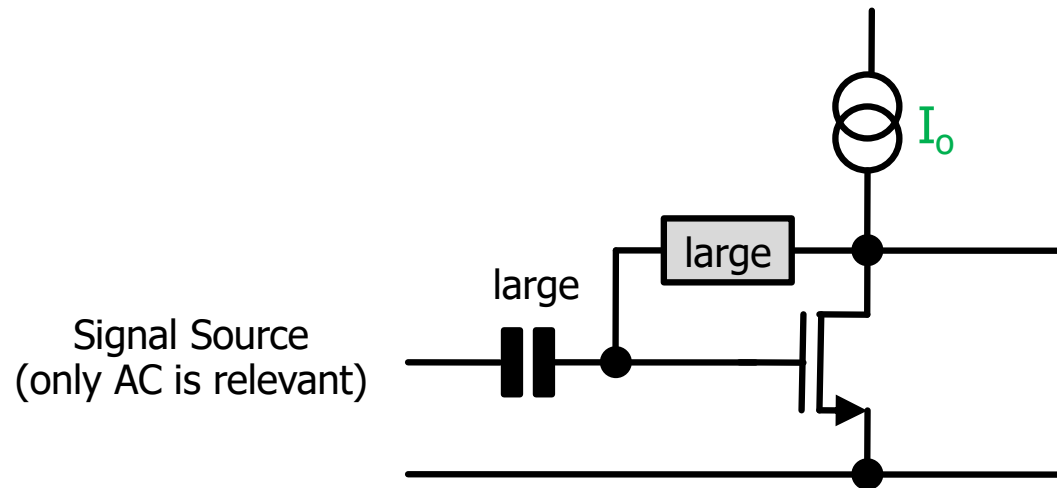
## Biassing the Gain Stage

- In practice (& in simulation),  $V_{GS}$  and  $I_0$  must 'correspond'
- This can be achieved (for instance) by a 'diode' connection of the MOS
- In simulation: To *let signals pass through*, the connection is done with a very large resistor and the input signal is ac coupled with an 'infinite' capacitor.




- In practice, other methods can be used...



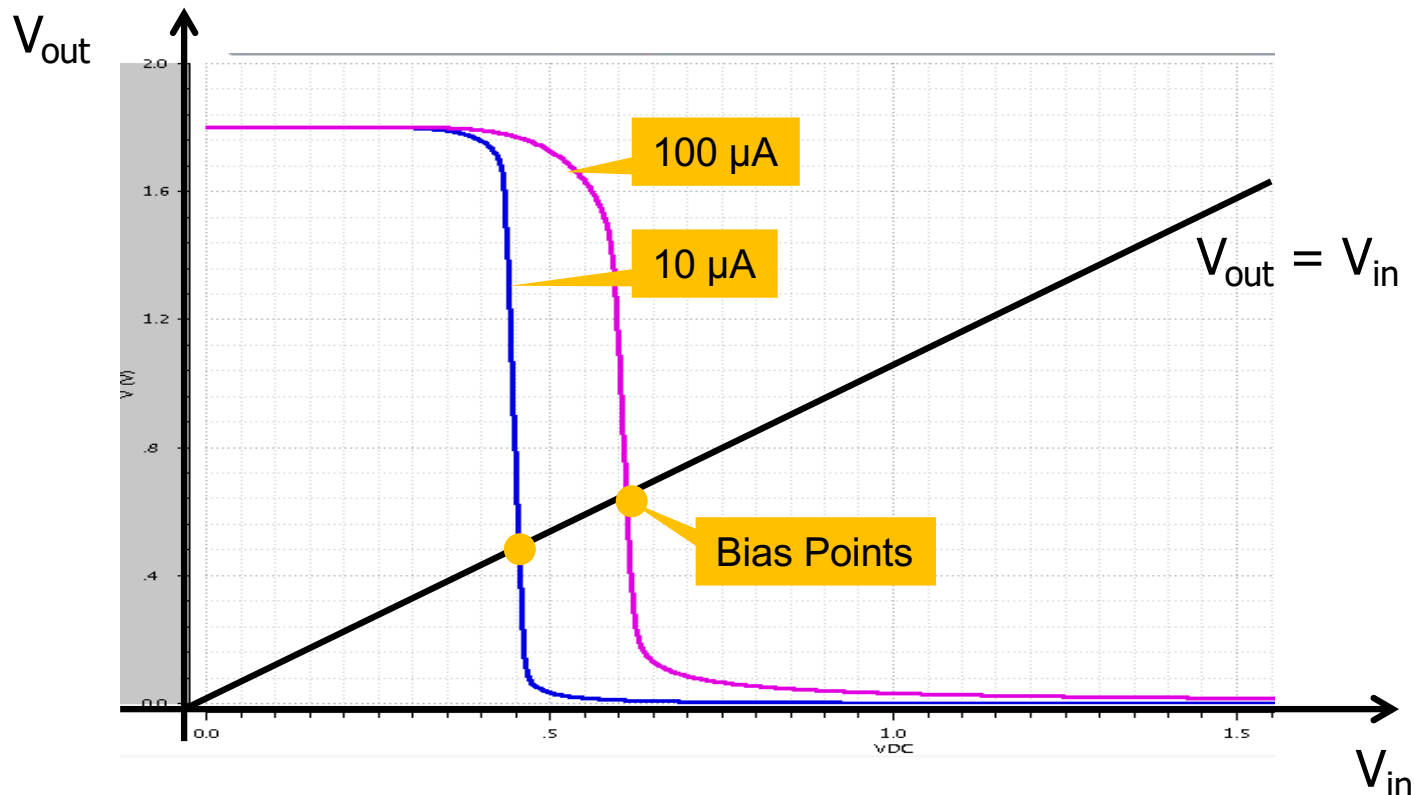
# Another View on the Bias Problem

- The resistor on the previous page forces  $V_{out} = V_{in}$
- The operation point is the crossing between the *diagonal* ( $V_{out} = V_{in}$ ) and the *transfer characteristic*
- This is usually a good point (maybe a bit low...)
- This works 'automatically' for changing bias & geometry





# How about a Resistive Load?

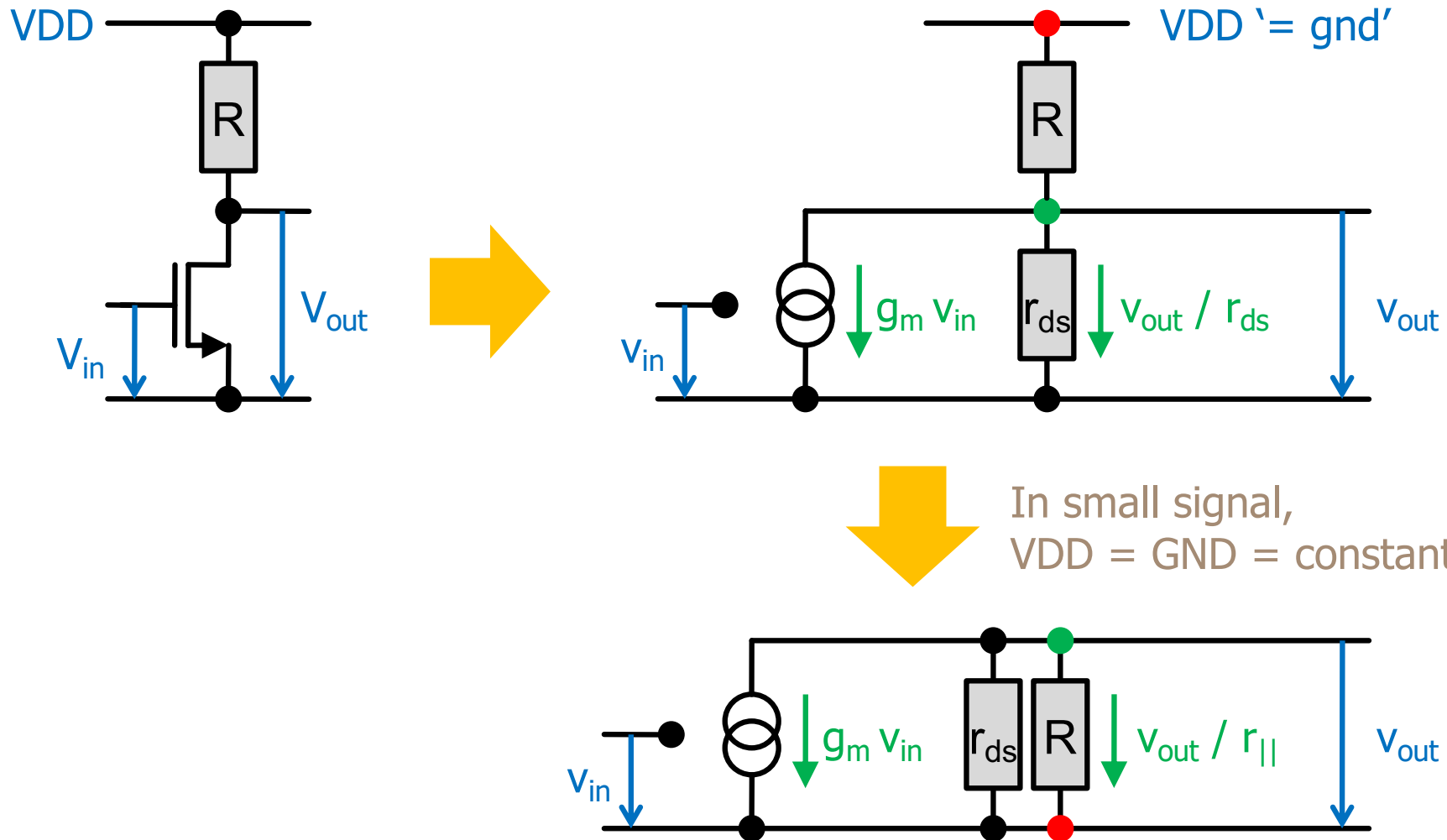


→  $R$  and  $r_{ds}$  act in parallel:  $v = -g_m \times (r_{ds} \parallel R)$




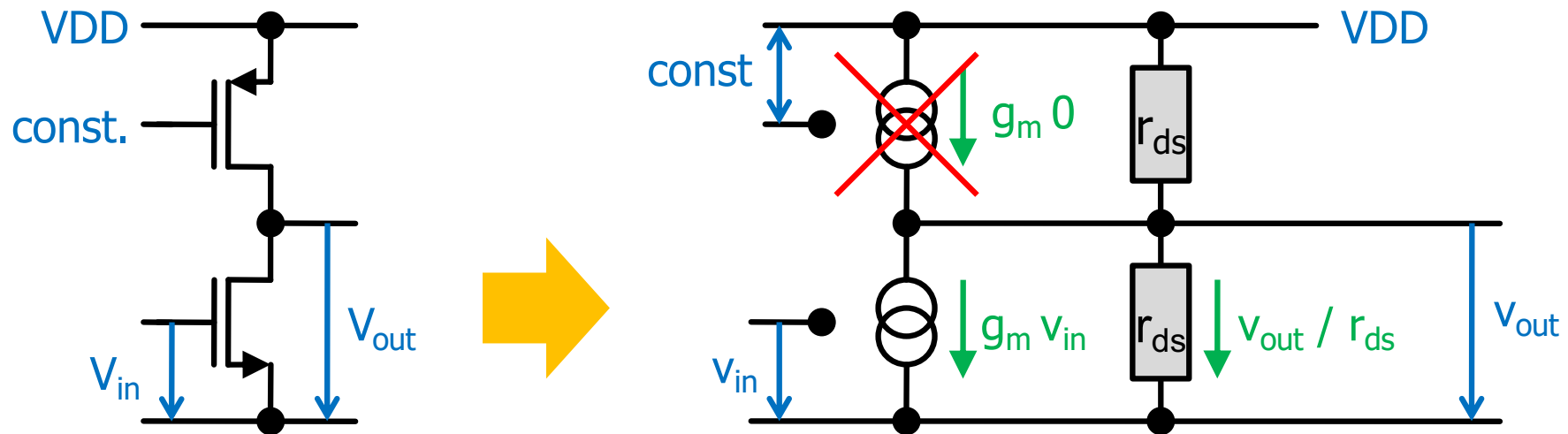
# Non-Ideal (PMOS) current source


- When a PMOS is used as current source, it ALSO has an output resistance.



- The transconductance part of the PMOS is off ( $v_{gs} = 0$ )
- The PMOS behaves just like a pure resistor (but  $r_{ds}$  is usually higher when in saturation)




# Reminder: Transistor Characteristics

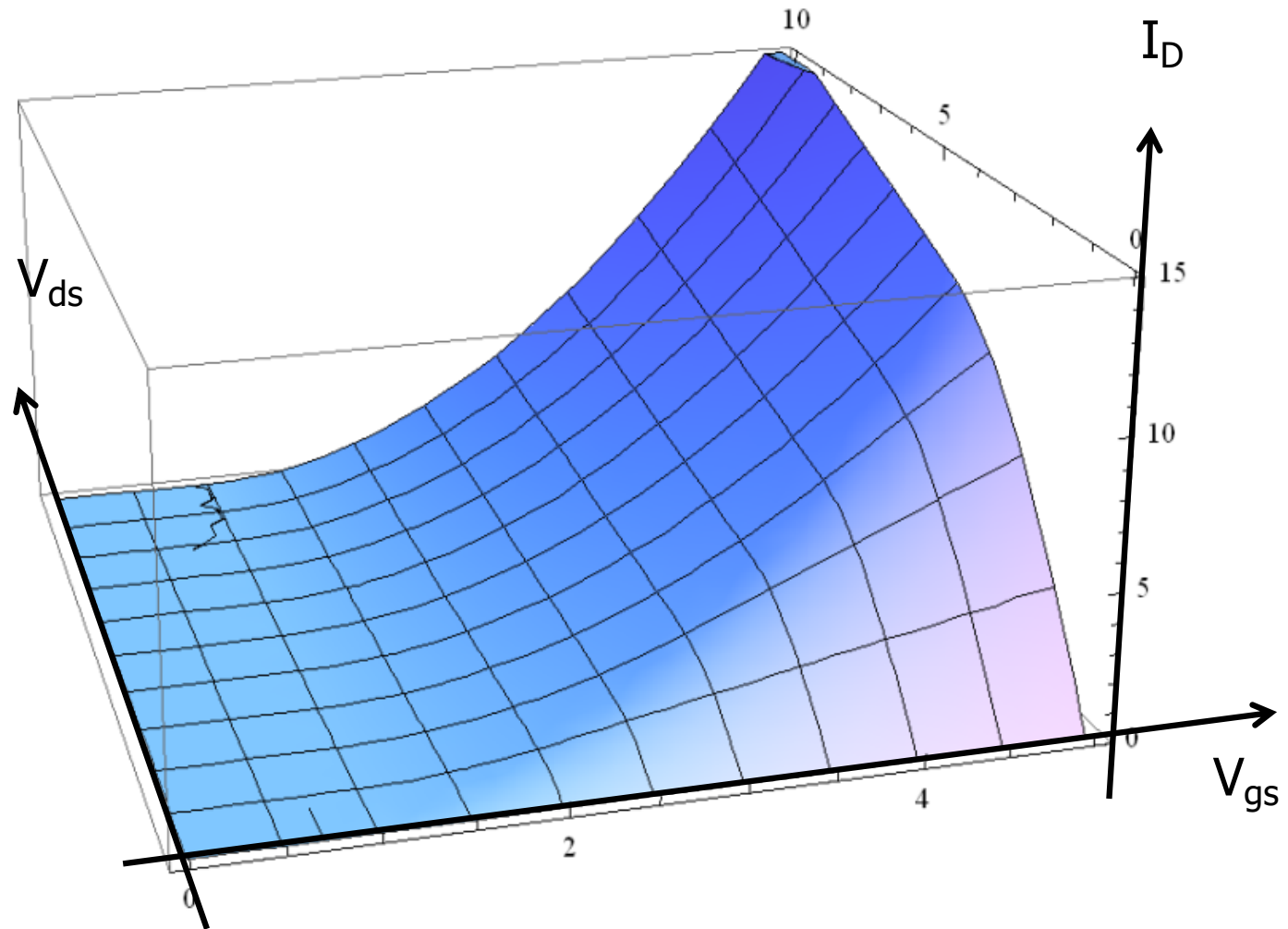



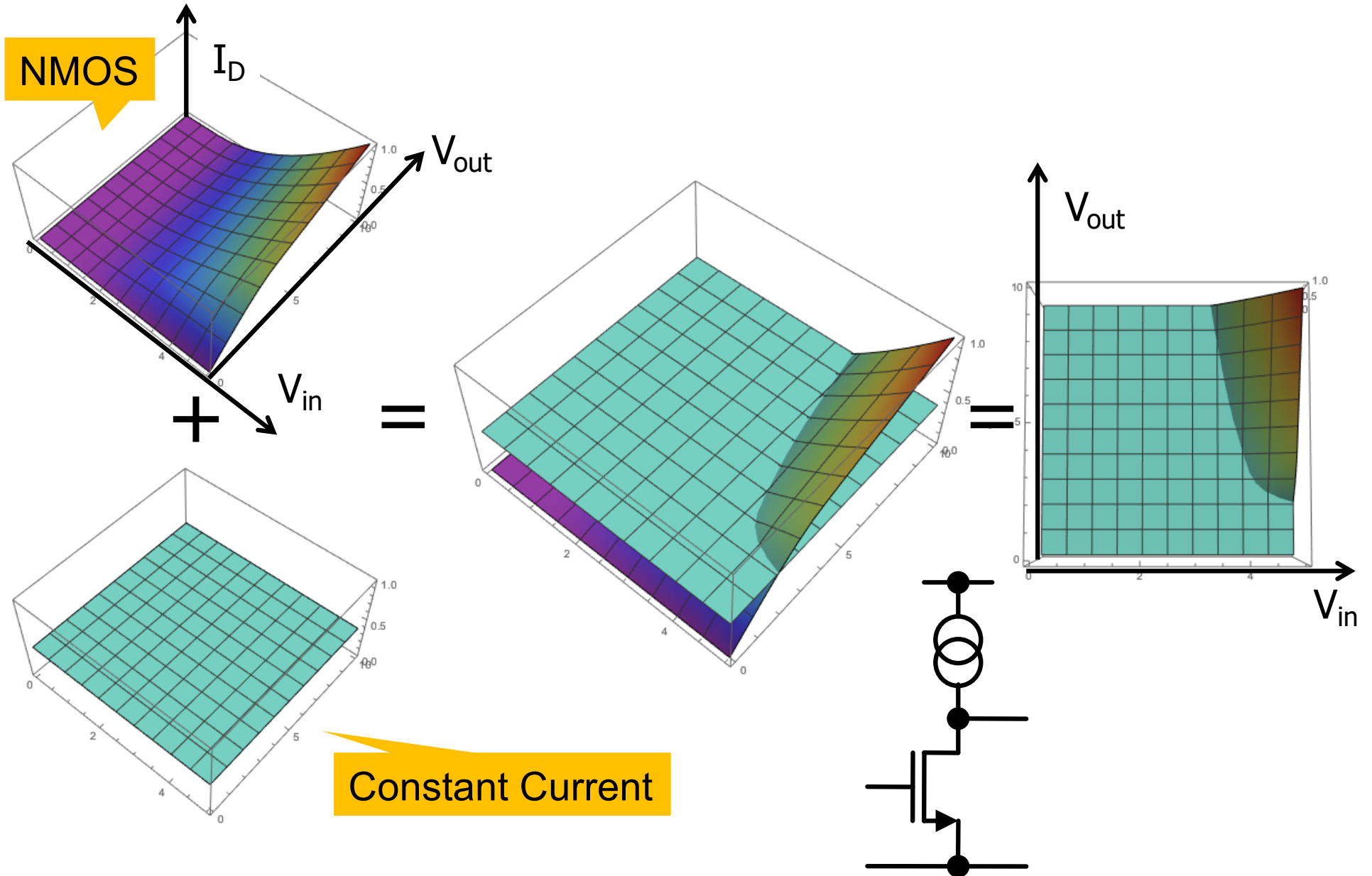
# Visualization of Transfer Function: I-Load









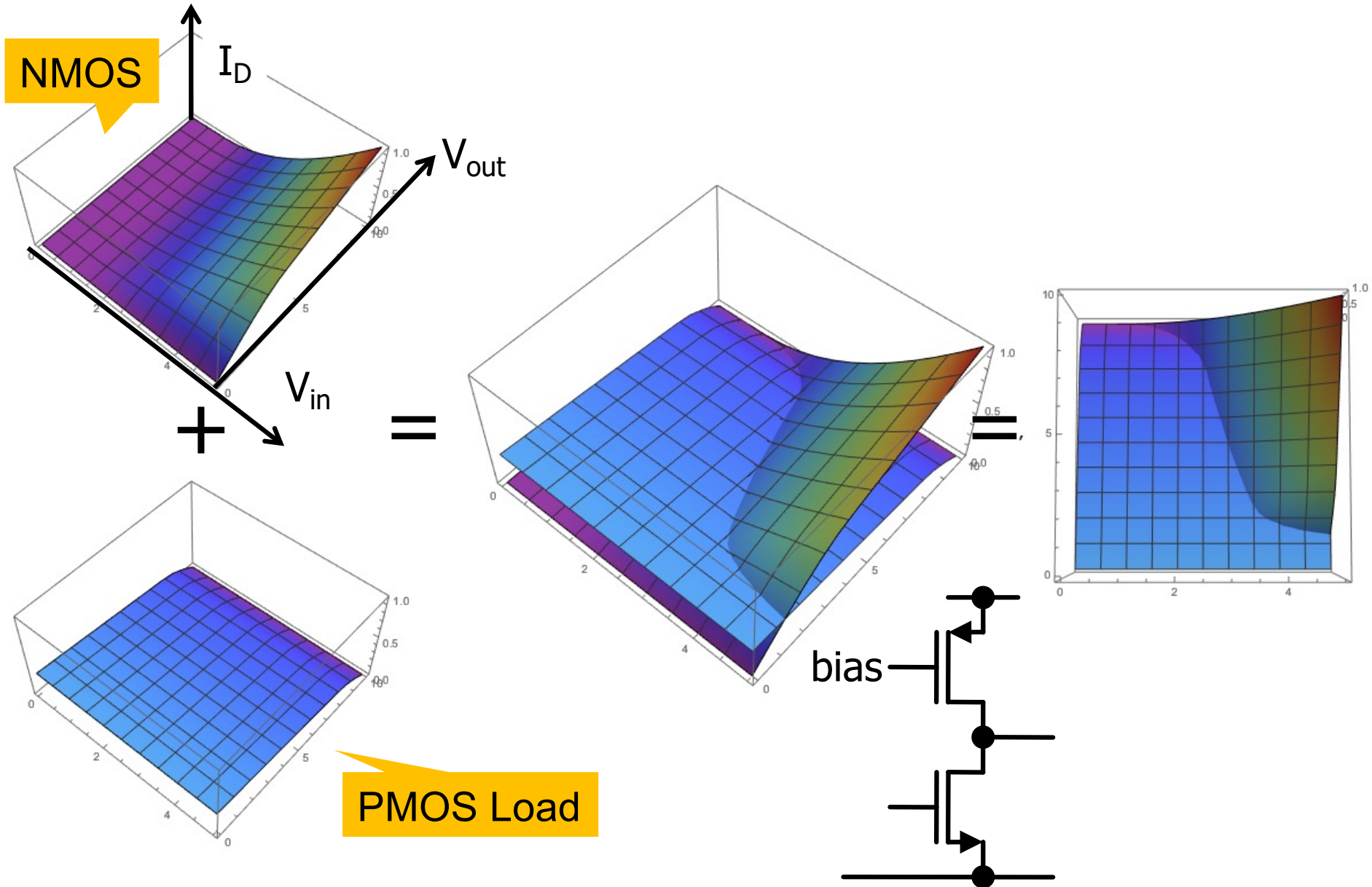
# Visualization of Transfer Function: PMOS Load







# Load = Diode Connected (N)MOS

     






# Visualization of Transfer Function: Inverter

NMOS

 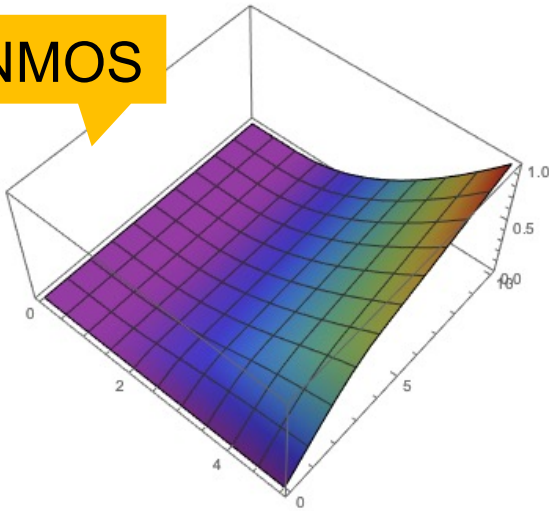


Active PMOS

   



# CMOS Inverter

- Now consider a CMOS inverter:

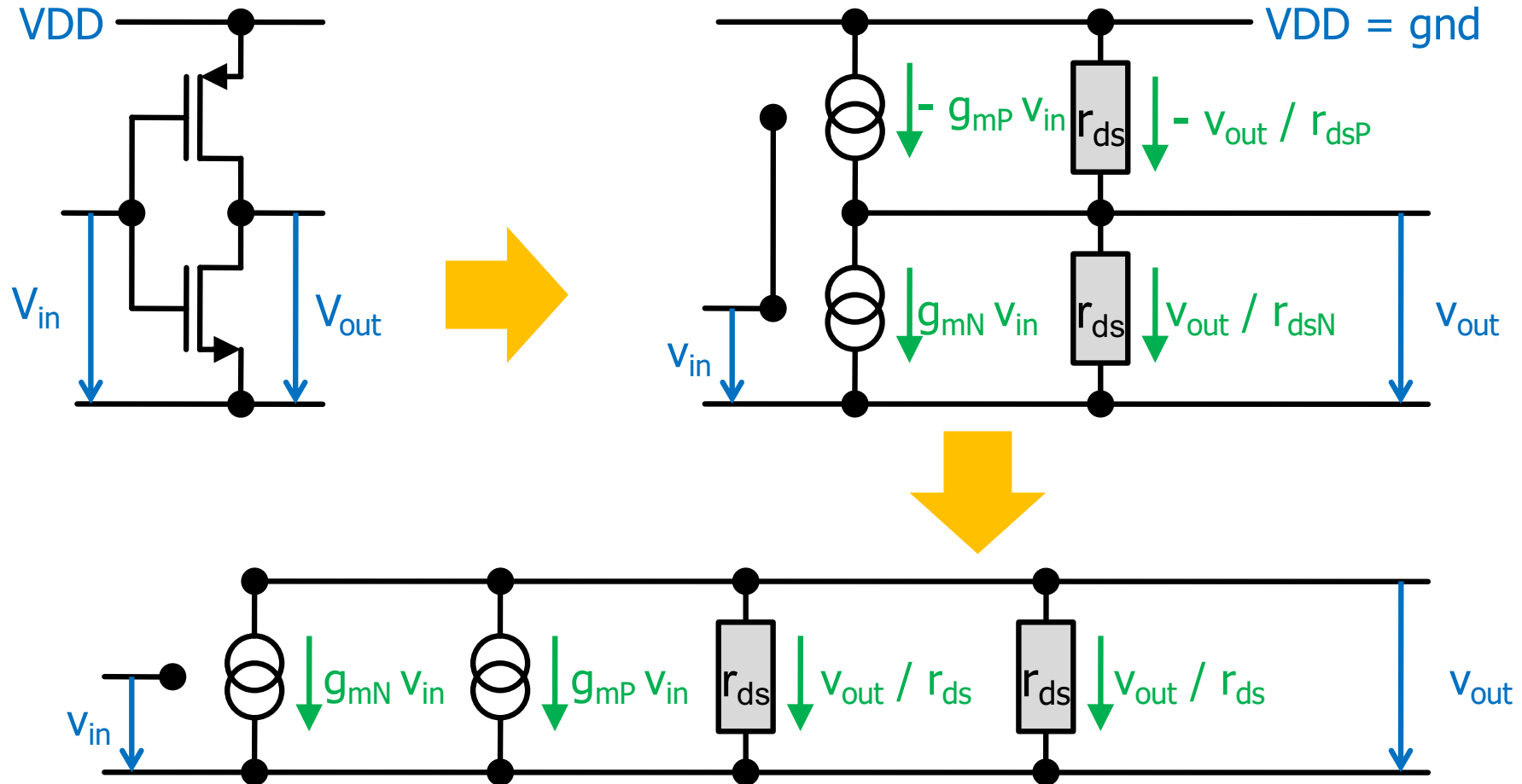

- $g_m$  and  $r_{ds}$  of both MOS are in **parallel**  

$$v = - (g_{mN} + g_{mP}) \times (r_{dsN} \parallel r_{dsP})$$




# INCREASING THE GAIN




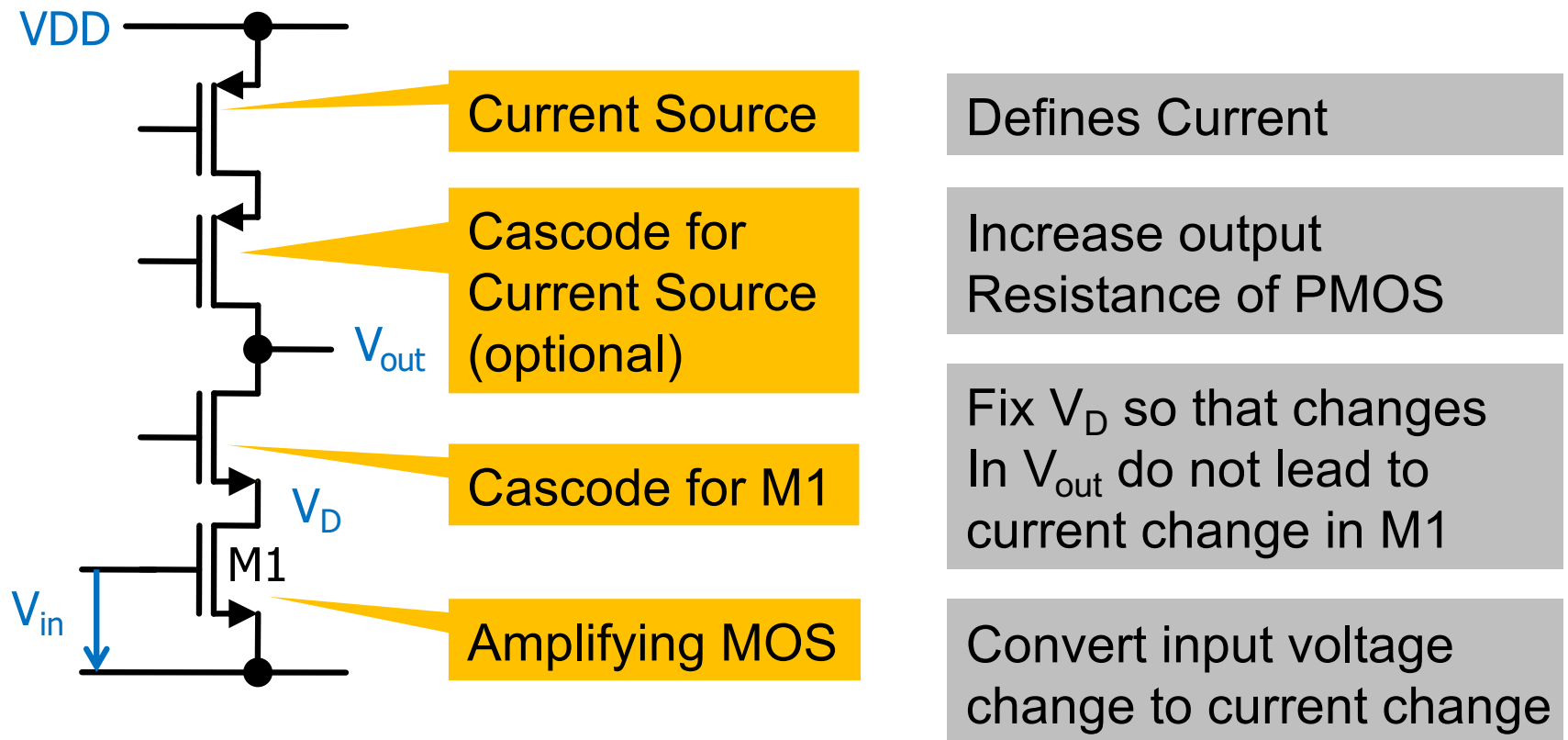
# How to get very high gain ?


- $g_m$  is very much limited by the current (can increase  $W...$ )
- $r_{ds}$  can be increased by a cascode
- This leads to the 'straight' cascode gain stage:




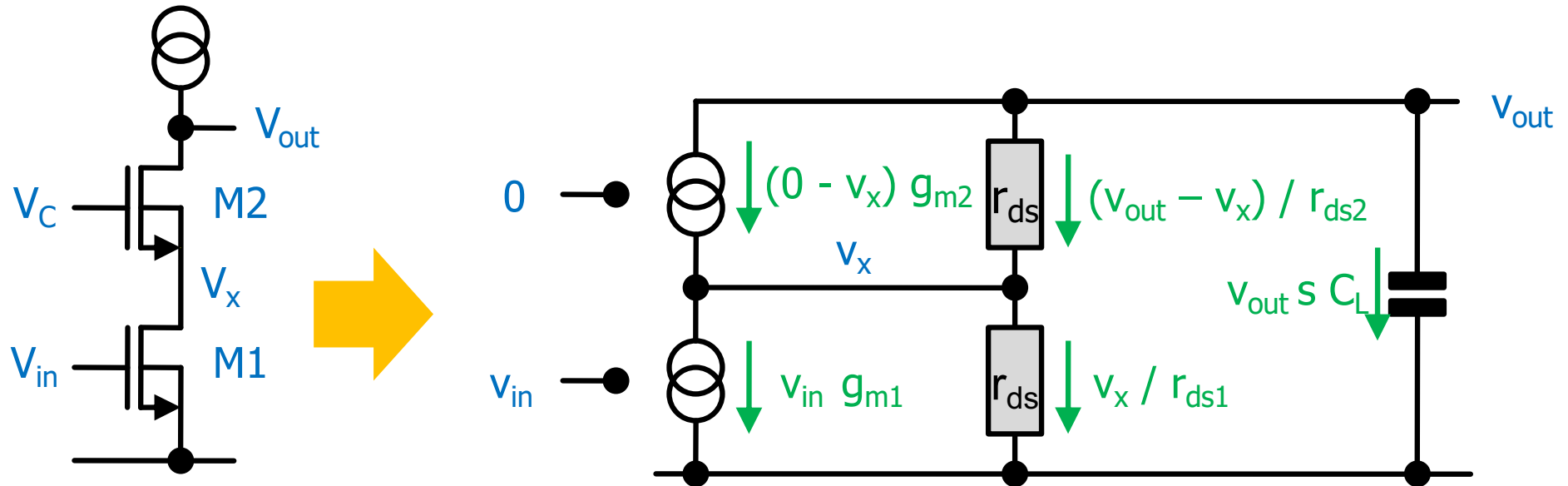
# Small Signal Analysis

- Assume bulks are connected to sources (no substrate effect)
  - Not always true in reality when NMOS are used...



- EQ1 (current sum at node  $v_{out}$ ):
 
$$-v_x g_{m2} + (v_{out} - v_x) / r_{ds2} + v_{out} s C_L = 0$$
- EQ2 (current sum at node  $v_x$ ):
 
$$-v_x g_{m2} + (v_{out} - v_x) / r_{ds2} = v_{in} g_{m1} + v_x / r_{ds1}$$





# Solution

- $$H(s) = - \frac{g_{m1} r_{ds1} (1 + g_{m2} r_{ds2})}{1 + C_L (r_{ds1} + r_{ds2} + g_{m2} r_{ds1} r_{ds2}) s}$$
- As usually  $g_m r_{ds} \gg 1$ , the parenthesis can be simplified:
- $$H(s) \sim - \frac{g_{m1} r_{ds1} g_{m2} r_{ds2}}{1 + C_L g_{m2} r_{ds1} r_{ds2} s} \quad (= \text{single pole low pass})$$
- The *DC gain* is  $|H(0)| = g_{m1} r_{ds1} \times g_{m2} r_{ds2}$   
(i.e. *squared* wrt. a simple gain stage!)
- The bandwidth is  $BW = (C_L r_{ds1} \times g_{m2} r_{ds2})^{-1}$   
(*decreased* by same factor)
- The unity gain bandwidth is the **same** as simple stage!  
 $GBW = BW \times |H(0)| = g_{m1}/C_L$




# DC Sweep

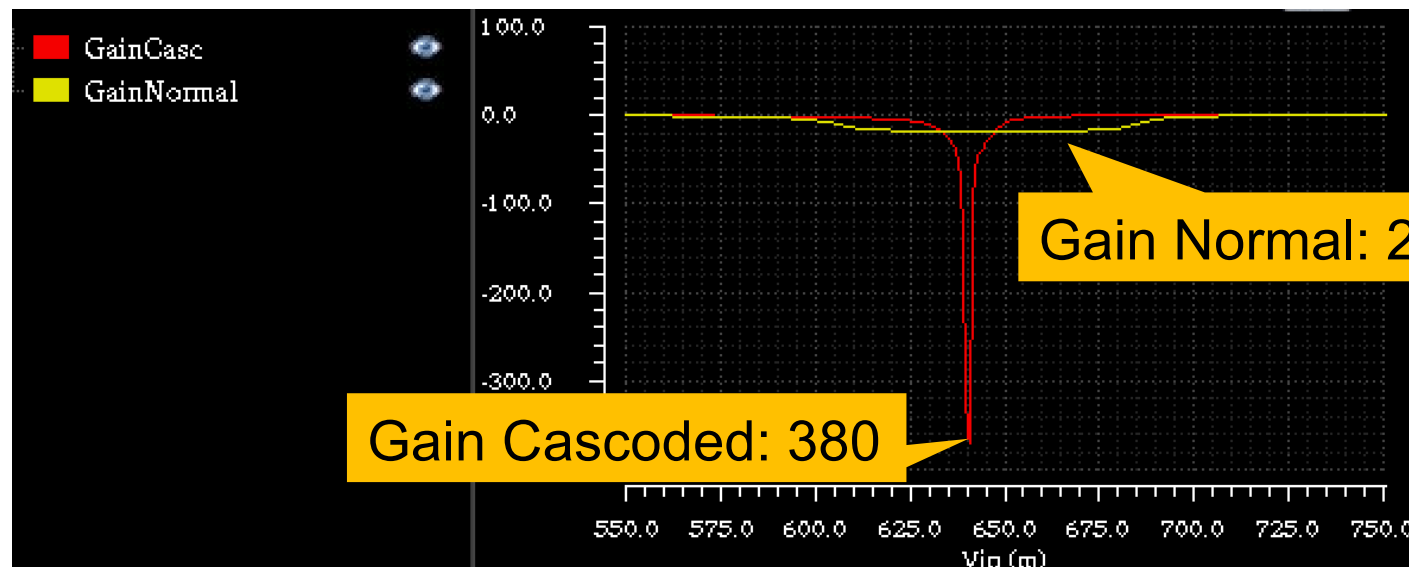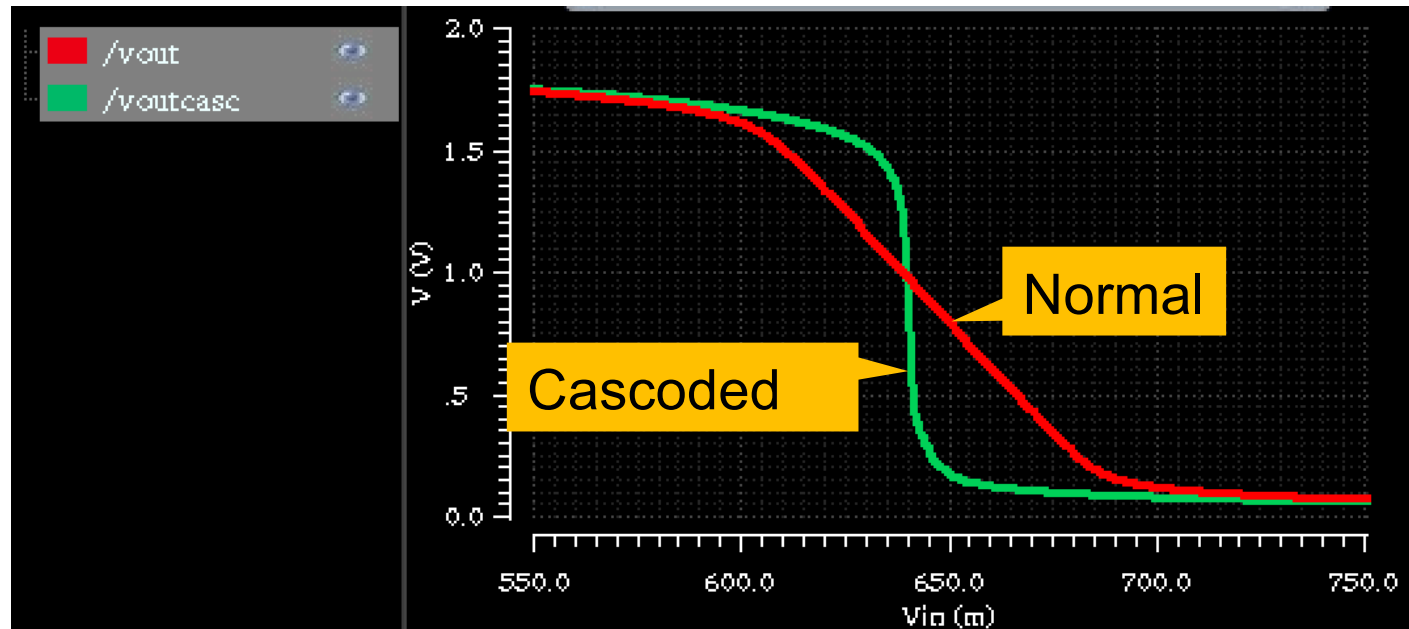


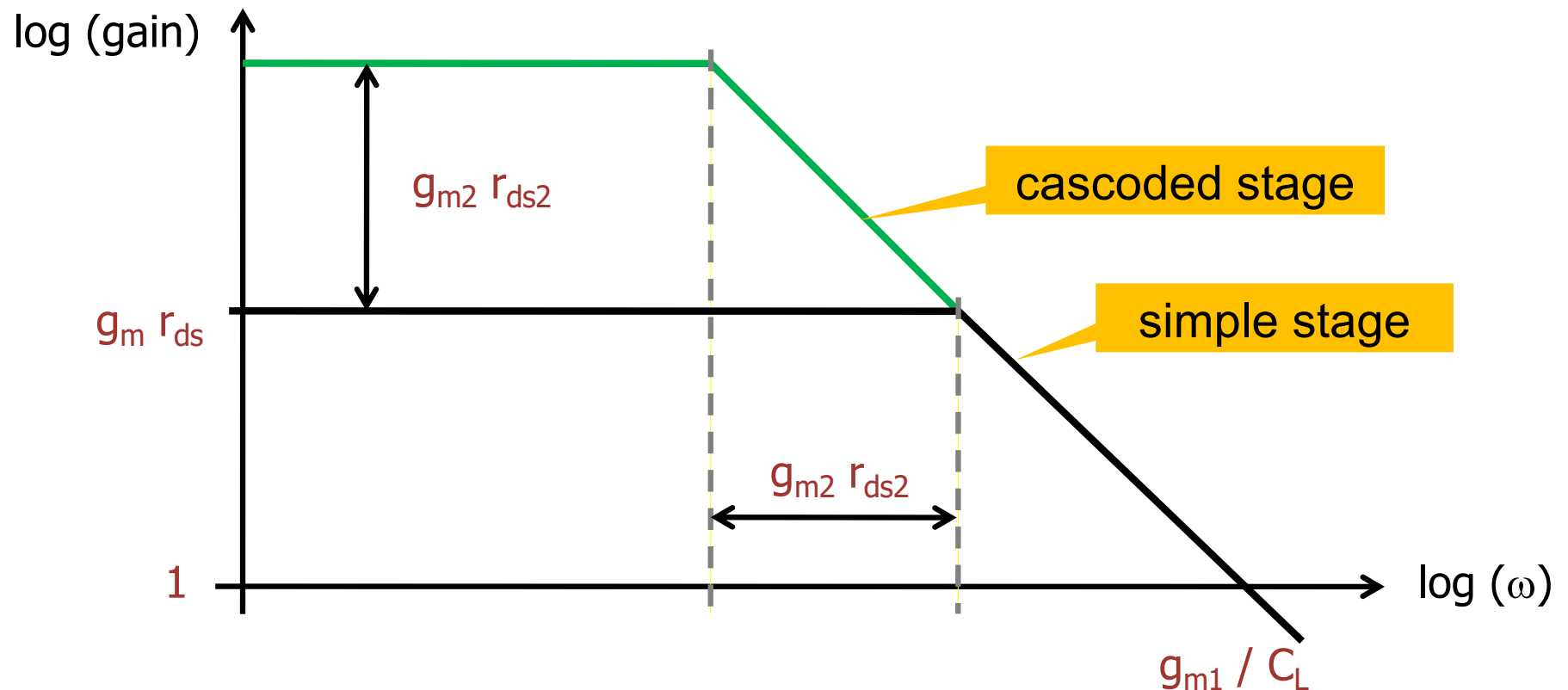
# Comparing Simple / Cascoded Gain Stage


- DC gain is increased by the 'gain'  $g_m \times r_{ds}$  of the cascode
  - the cascode 'boosts' the output resistance
- The GBW remains *unchanged* 😞
  - the current generated in M1 must charge  $C_L$ . The cascode does *not* help for speed ... We need more  $g_m \rightarrow$  more power




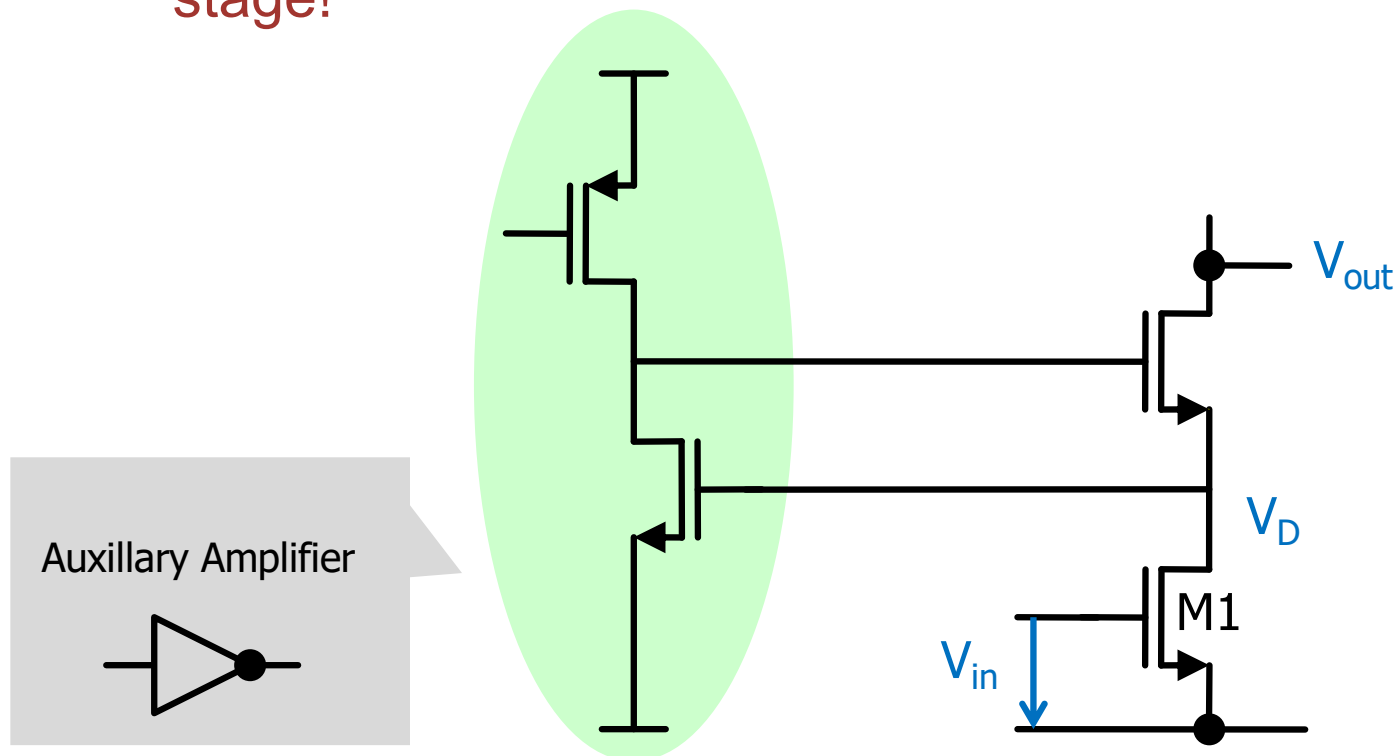
## How to get EVEN higher gain ?


- Just like we have done in the 'regulated' mirror, we can use an amplifier to keep the drain of the amplifying MOS at constant potential.
- For the amplifier, we use (again) a simple gain stage...
- With this method, a gain of 10.000 can be reached in one stage!




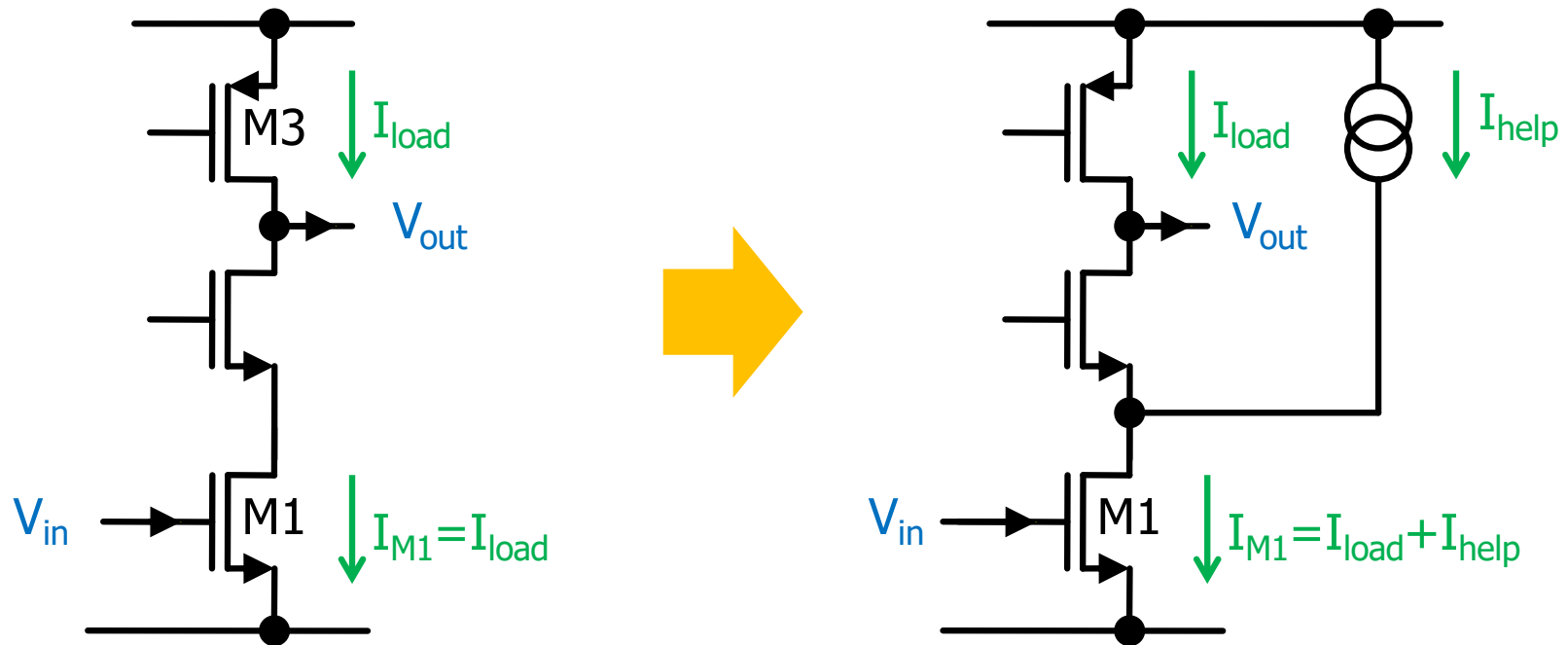
# Increasing gain further


- The gain (left) is limited by the output cond. of the load M3
  - That is proportional to the current in the load
- Can we *reduce* the current in the *load*, keeping the current in the amplifying MOS M1 unchanged (for  $g_m$ )?
- Yes: Add an extra current to M1 at the cascode node:




 
## For Experts: The 'folded' cascode

- The 'straight' cascode has some drawbacks
  - many MOS are stacked  $\rightarrow$  dynamic range suffers
  - DC feedback ( $v_{out} = v_{in}$ ) is marginal as  $v_{out}$  cannot go very low
- Alternative: use a PMOS to cascode the input NMOS M1:
  - Quite surprising that this works....



- Current in output branch is smaller than in M1  $\rightarrow r_{out}$  is higher
- Note: It may *look* like this topology has non-inverting gain...







# ADVANCED TOPICS


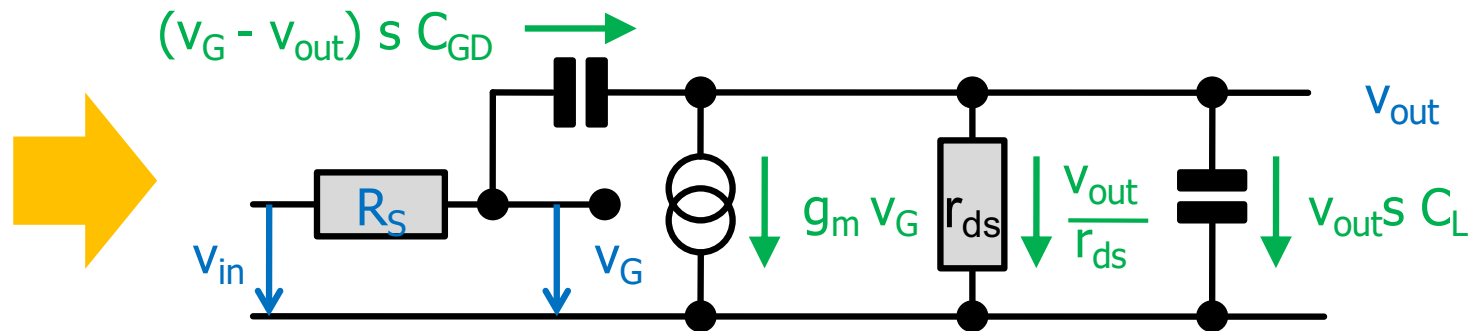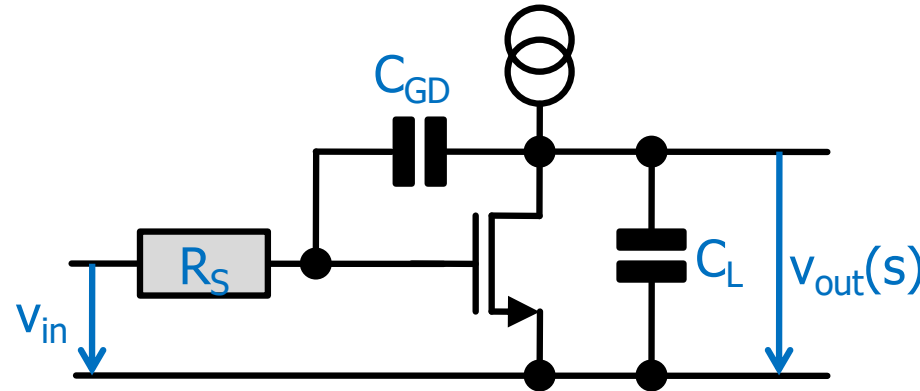
# $C_{GD}$ : Introducing a 'Zero' (Advanced Topic)

- Consider the effect of the gate-drain capacitance  $C_{GD}$ 
  - Assume a finite driving impedance of the source  $R_S$ :




$$H(s) = \frac{-g_m r_{ds} + C_{GD} r_{ds} s}{1 + C_L r_{ds} s + C_{GD} s (r_{ds} + R_S + g_m r_{ds} R_S + C_L r_{ds} R_S s)}$$


 
# New: We get a Zero - What Happens?



- We have  $H(0) = -g_m r_{ds}$  as before.
- For  $R_S=0$ 
  - The input signal propagates directly to the output via  $C_{GD}$ .
  - This same phase signal competes with the inverted signal through the MOS.
  - For very large frequencies,  $C_{GD}$  'wins'.
  - We therefore have zero gain at some point
  - At high frequencies, we have a capacitive divider with gain  $< 1$




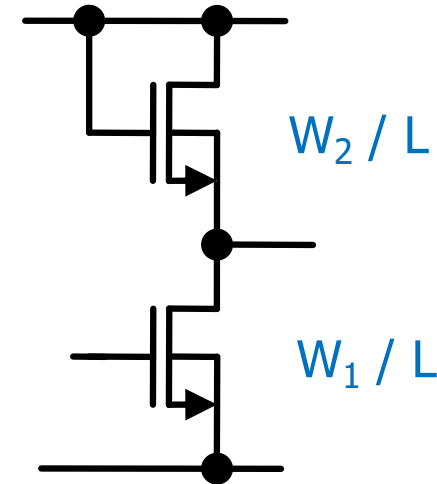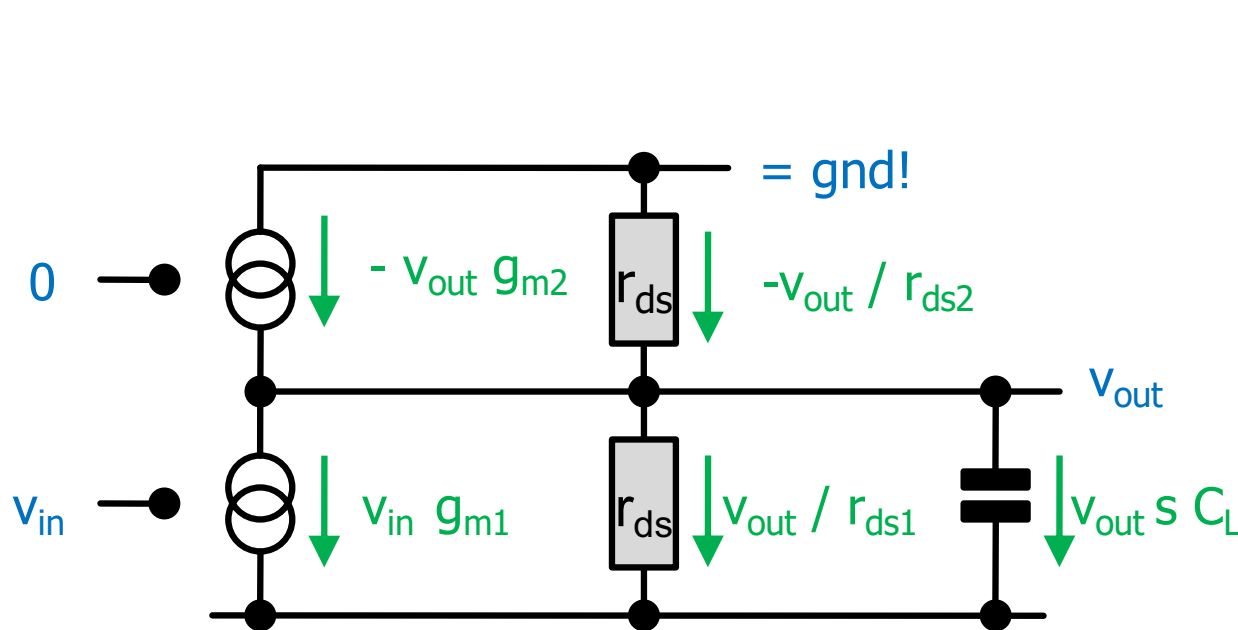
# Check your Understanding:

- What is  $H(s)$  of a gain stage with a (NMOS) diode load:



- $$H(0) = - \frac{g_{m1} r_{ds1} r_{ds2}}{r_{ds1} + r_{ds2} + g_{m2} r_{ds1} r_{ds2}} \sim - \frac{g_{m1}}{g_{m2}}$$

- In strong inversion, this is the square root of the  $W$ -ratio
  - For instance: for  $W_2 / W_1 = 4$ , the gain is  $\sim 2$ .




# THE CURRENT MIRROR - AGAIN


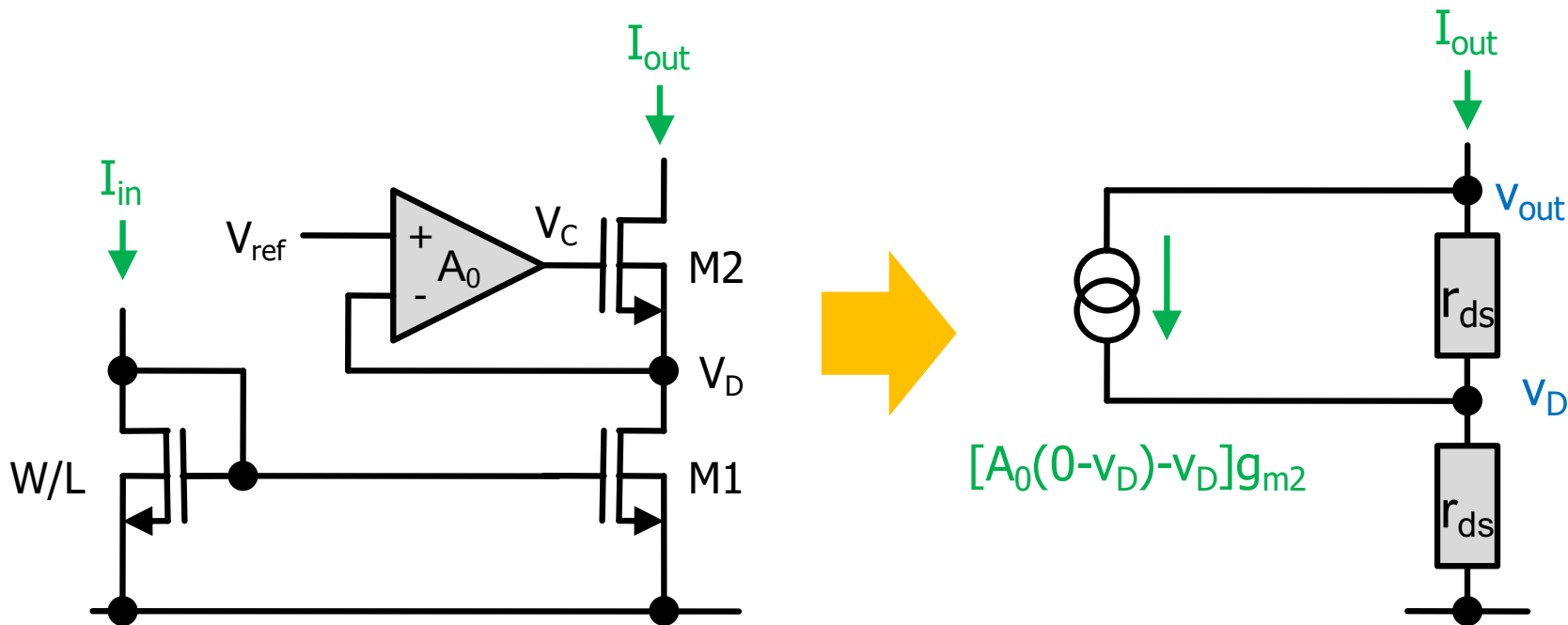
# Active Regulation of the Drain Voltage

- The following circuit uses an amplifier with gain  $A_0$  to keep  $V_D$  constant:
  - $V_D$  is compared to a (fixed) reference  $V_{ref}$ .
  - $V_C = A_0 (V_{ref} - V_D)$
- For better *matching*, the input must be cascoded as well..




$$r_{out} = r_{ds2} + r_{ds1} (1 + (1 + A_0) g_{m2} r_{ds2})$$


 
# Practical Realization

- The amplifier can just be a gain stage...
- This gives the ‚regulated current mirror‘:



- Here,  $A_0 \sim g_{m3} r_{ds3}$ , Therefore  $r_{out} \sim r_{ds1} \times g_{m2} r_{ds2} \times g_{m3} r_{ds3}$
- Note:
  - $V_{DS}$  of M1 is  $\sim V_{TN}$ , which is higher than needed (wasting dyn.). (Using M3 with lower threshold helps)
  - Matching is *not* good, because  $V_{DS0} \neq V_{DS1}$  -> add left cascode